



Principle of EE1

Lesson 3

Prof. Võ Văn Tới

School of Biomedical Engineering

Vice-Provost for Life and Health Science, Engineering and Technology Development


International University

Vietnam National Universities – HCMC

OTHER METHODS OF ANALYZING RESISTIVE CIRCUITS

1. MESH CURRENT ANALYSIS

Principle

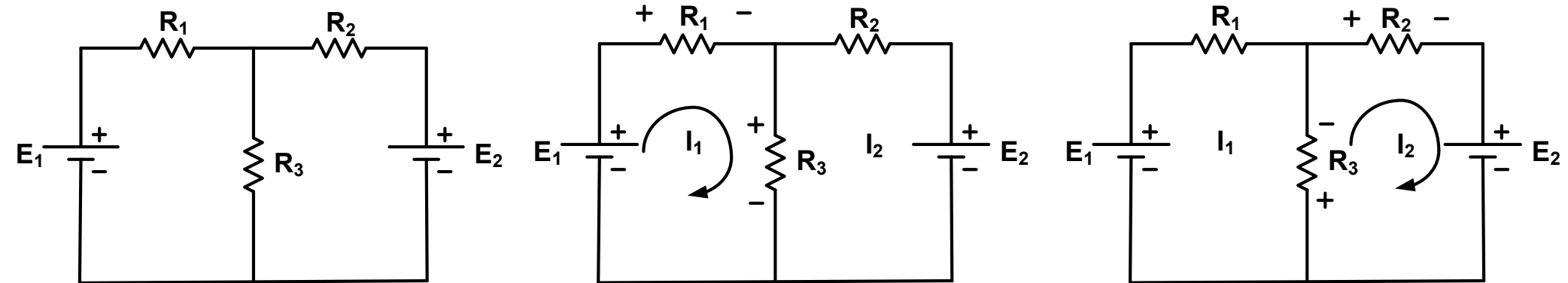

Principle

Kirchhoff's voltage laws for each mesh:

$$\text{Mesh 1: } -E_1 + R_1 I_1 + R_3 I_1 - R_3 I_2 = 0 \quad (1)$$

$$\text{Mesh 2: } R_3 I_2 + R_2 I_2 + E_2 - R_3 I_1 = 0 \quad (2)$$

$$(1) \Rightarrow (R_1 + R_3) I_1 - R_3 I_2 = E_1 \quad (1')$$

$$(2) \Rightarrow -R_3 I_1 + (R_3 + R_2) I_2 = -E_2 \quad (2')$$


Statement: $\sum V$ of the loads = $\sum V$ of the sources \Leftrightarrow Ohm's law

(1'): Sum of resistances in mesh 1 * current of mesh 1 – Common resistance * current of the mesh 2 = Voltage of the source of mesh 1

(2'): Sum of resistances in mesh 2 * current of mesh 2 – Common resistance * current of the mesh 1 = - Voltage of the source of mesh 2

Rules:

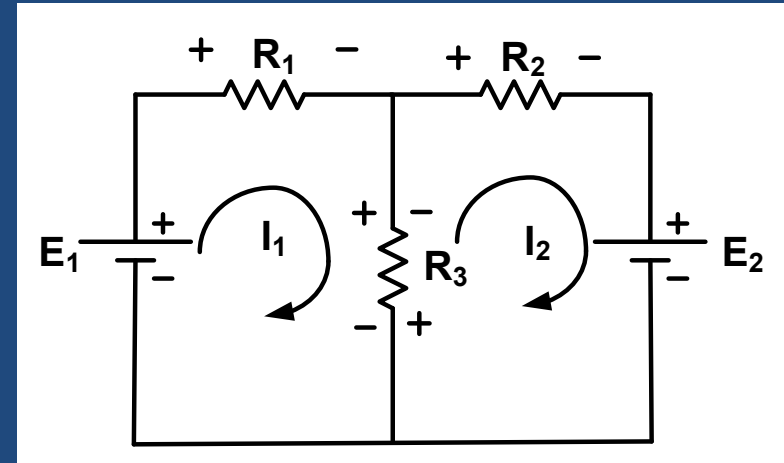
1. Select the currents for each mesh: They must be in the same direction
2. Establish equation like (1') and (2') for each mesh. Attention: relation between mesh current direction and source voltage polarity



Situations and corresponding methods

- i. Circuits with only voltage sources
- ii. Circuits with voltage source and current sources in the outside meshes
- iii. Circuits with voltage source and current source between the meshes => Super-mesh

Example 1

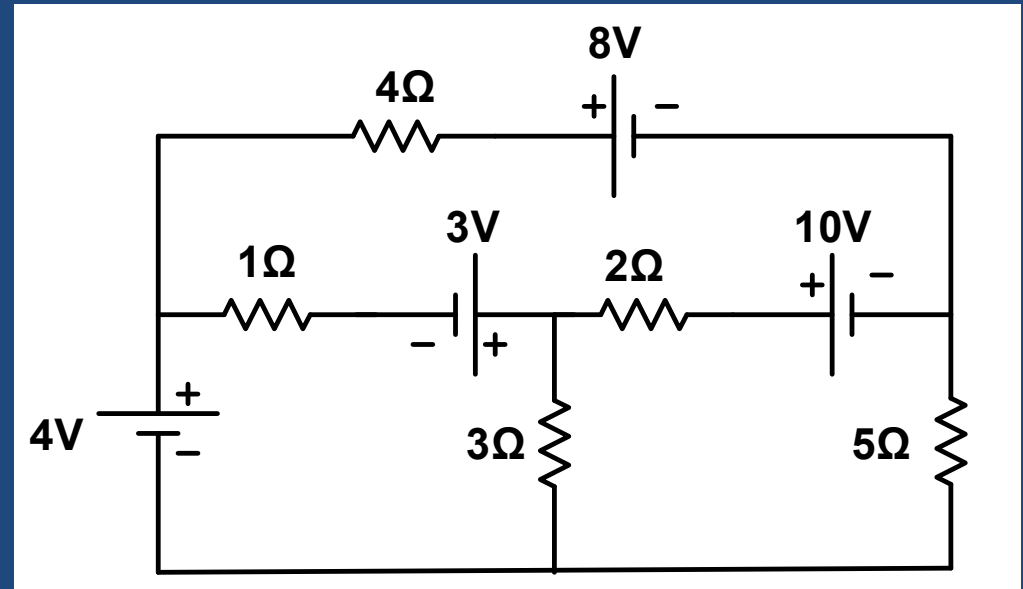

Determine the currents through $4V$, $8V$ and $3V$ sources, and 3Ω resistor

Solution of example 1

1. Give currents for each mesh

2. Equation of each mesh

$$\text{M1: } (1+3)I_1 - 3I_2 - I_3 = 4 + 3 \quad (1)$$

$$\text{M2: } -3I_1 + (3+2+5)I_2 - 2I_3 = -10 \quad (2)$$

$$\text{M3: } -I_1 - 2I_2 + (4+1+2)I_3 = 10 - 3 - 8 \quad (3)$$


3. $\Rightarrow I_1 = 1.2\text{A}; I_2 = -0.67\text{A}; I_3 = -0.16\text{A}$

4. Currents through $4\text{V} = I_1 = 1.2\text{A} \uparrow$


5. Currents through $8\text{V} = I_3 = -0.16\text{A}$ or Currents through 8V is $0.16\text{A} \leftarrow$

6. Currents through $3\text{V} = I_1 - I_3 = 1.2 + 0.16 = 1.36\text{A} \rightarrow$

7. Currents through $3\Omega = I_1 - I_2 = 1.2 + 0.67 = 1.87$
A \downarrow

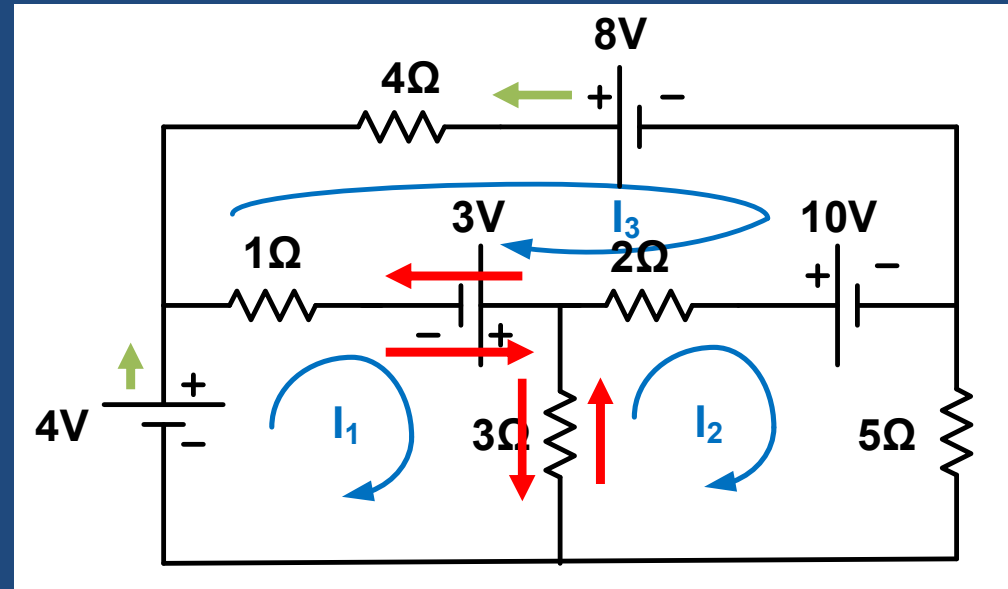


Example 2

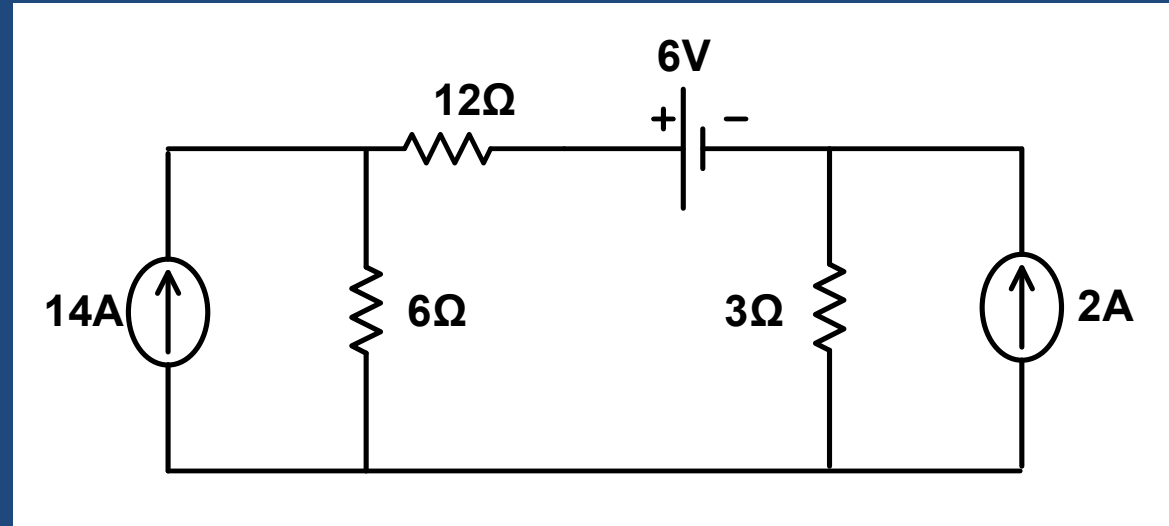

Determine the currents through 3Ω resistor

Note: there are current sources in outside meshes

Solution of example 2

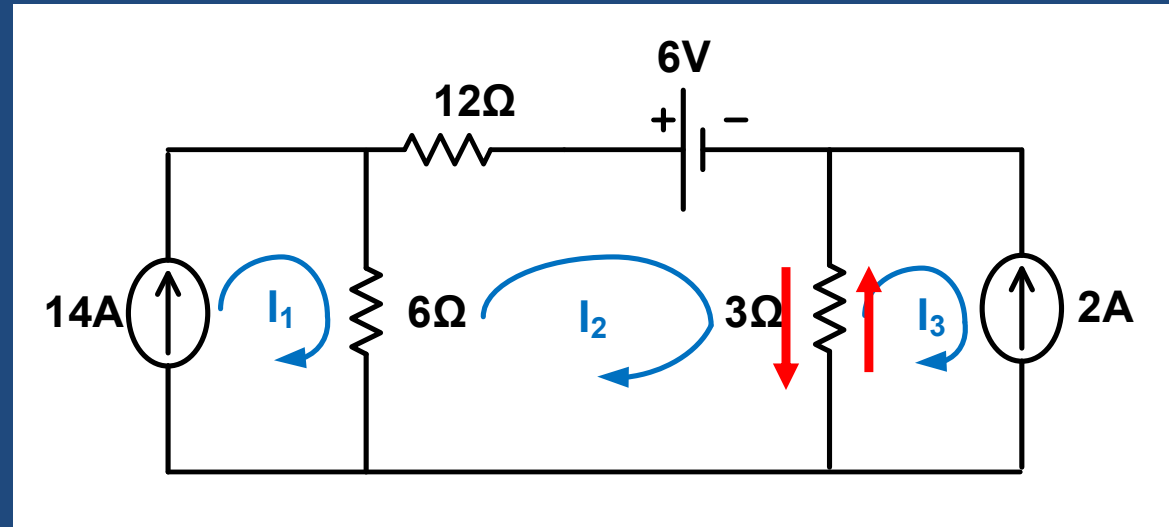

1. Give currents for each mesh

2. Equation of each mesh

- M1: $I_1 = 14$ (1)

- M2: $-6I_1 + (6 + 12 + 3)I_2 - 3I_3 = -6$ (2)


- M3: $I_3 = -2$ (3)

3. $\Rightarrow I_2 = 4 \text{ A}$

4. Currents through $3\Omega = I_2 - I_3 = 4 - (-2) = 6\text{A}$



Example 3

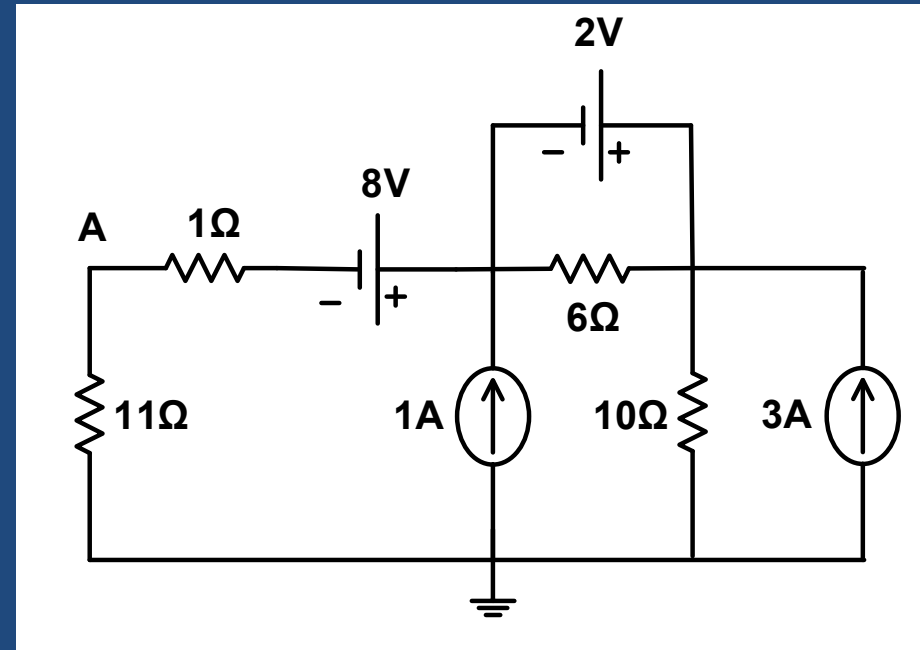


Determine the voltage V_A

Note: there is a current source between 2 meshes \Rightarrow super-mesh

Solution of example 3

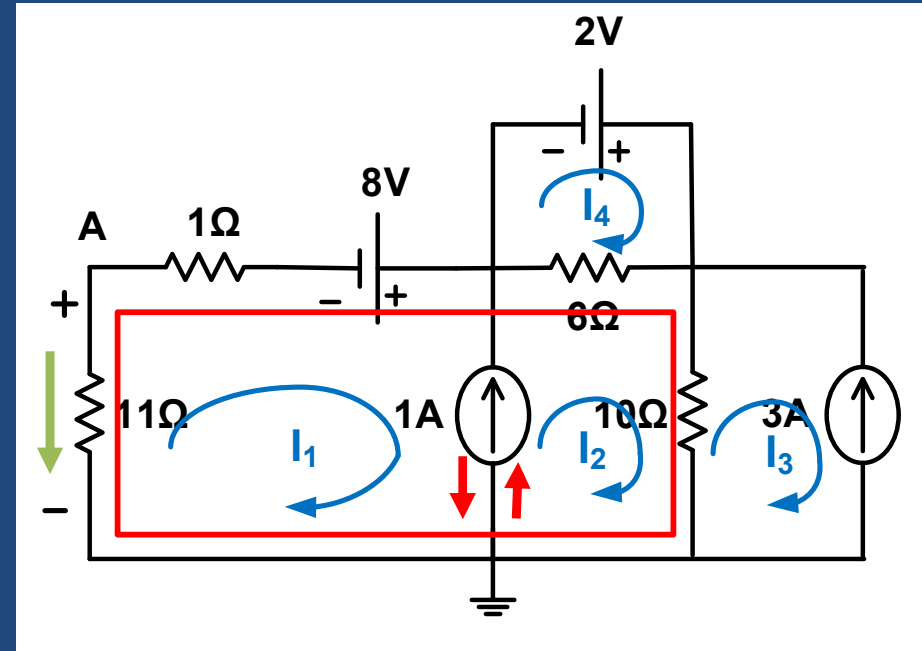1. Give currents for each mesh
2. Supermesh (1) and (2)
3. Equation of each mesh



- M1 + M2: $(11+1)I_1 + (6+10)I_2 - 10I_3 - 6I_4 = 8$ (1)

- M3: $I_3 = -3$ (2)

- M4: $-6I_2 + 6I_4 = 2$ (3)


- $I_2 - I_1 = 1$ (4)

4. $\Rightarrow I_1 = -1.4A; I_2 = -0.4A; I_4 = -0.07A$

5. $V_A = 11 \times 1.4 = \underline{15V}$

2. NODE VOLTAGE METHOD

Principle

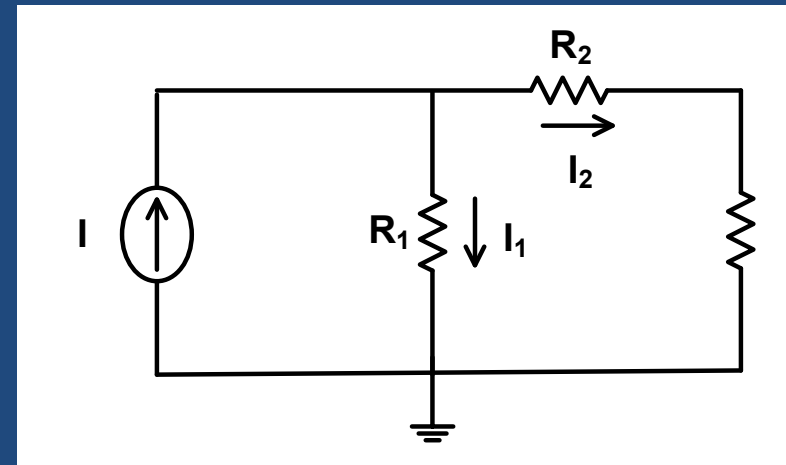


Principle

Kirchhoff's current laws for node A:

$$I_1 + I_2 = I$$

$$\frac{1}{R_1} V_A + \frac{1}{R_2} (V_A - V_B) = I \quad (1)$$
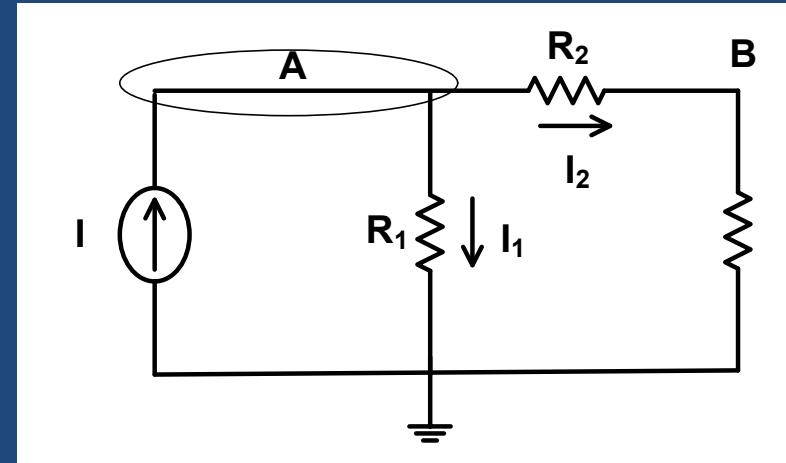
$$(1) \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_A - \frac{1}{R_2} V_B = I \quad (1')$$



Statement: ΣI of the sources = ΣI of the loads \Leftrightarrow Ohm's law

Sum of conductance at node A * voltage of A – Common conductance * voltage of B =
Current of the source that goes to A


Rules:

1. Identify all nodes and ground the biggest node
2. Establish equation like (1') for each node. **Attention:** direction of current source: positive if source goes in and negative if source goes out the node

Situations and corresponding methods

- i. Circuits with only current sources
- ii. Circuits with current sources and voltage source connected to ground
- iii. Circuits with current sources and voltage source between 2 nodes => Super-node

Example 4

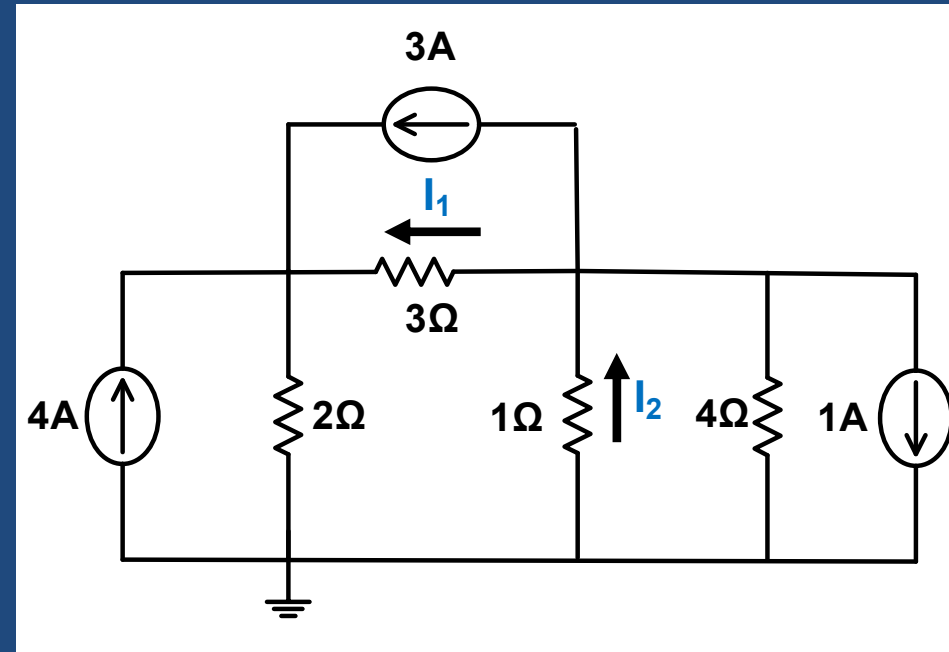

Determine the currents I_1 and I_2

Solution of example 4

1. Identify all nodes

2. Equation for each node


$$A: \left(\frac{1}{2} + \frac{1}{3}\right)V_A - \frac{1}{3}V_B = +3 \quad (1)$$

$$B: -\frac{1}{3}V_A + \left(1 + \frac{1}{3} + \frac{14}{4}\right)V_B = -3 - 1 \quad (2)$$

$$\Rightarrow V_A = 8.07V; V_B = -0.83V$$

$$\Rightarrow I_1 = \frac{V_B - V_A}{3} = \frac{-0.83 - 8.07}{3} = -\underline{\underline{3A}}$$


$$I_2 = \frac{-V_B}{1} = \underline{\underline{0.83A}}$$

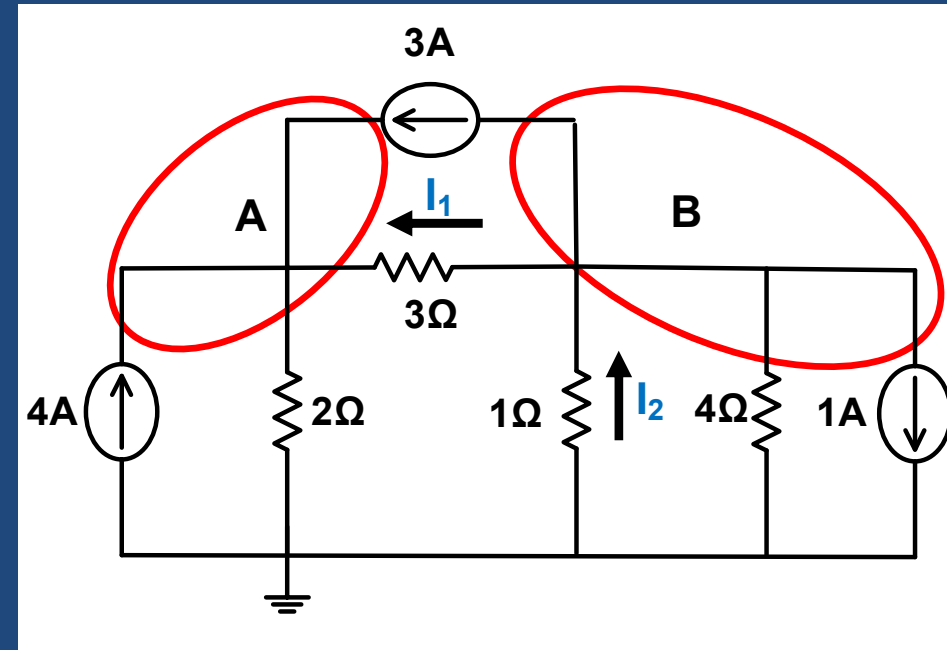

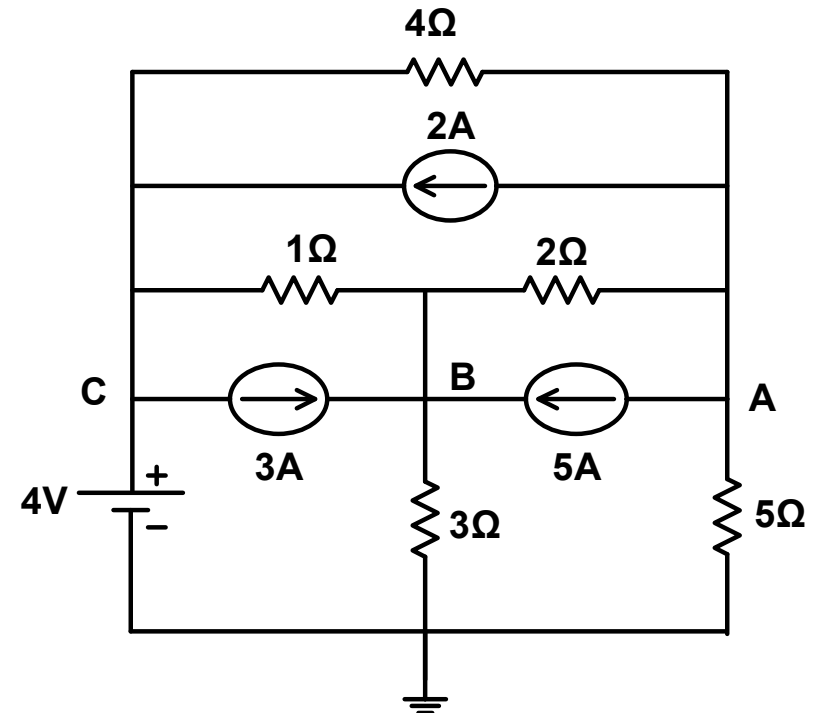Example 5

Determine the voltages V_A and V_B

Note: There is a voltage source with one polarity connected to the ground



Solution of example 5

1. Identify all nodes
2. Equation for each node


$$\text{A: } \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{5}\right) V_A - \frac{1}{2} V_B - \frac{1}{4} V_C = -2 - 5 \quad (1)$$

$$\text{B: } -\frac{1}{2} V_A + \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{3}\right) V_B - \frac{1}{1} V_C = 3 + 5 \quad (2)$$

$$\text{C: } V_C = 4$$


$$\Rightarrow V_A = \underline{\underline{-3.4V}}$$

$$V_B = \underline{\underline{5.6V}}$$

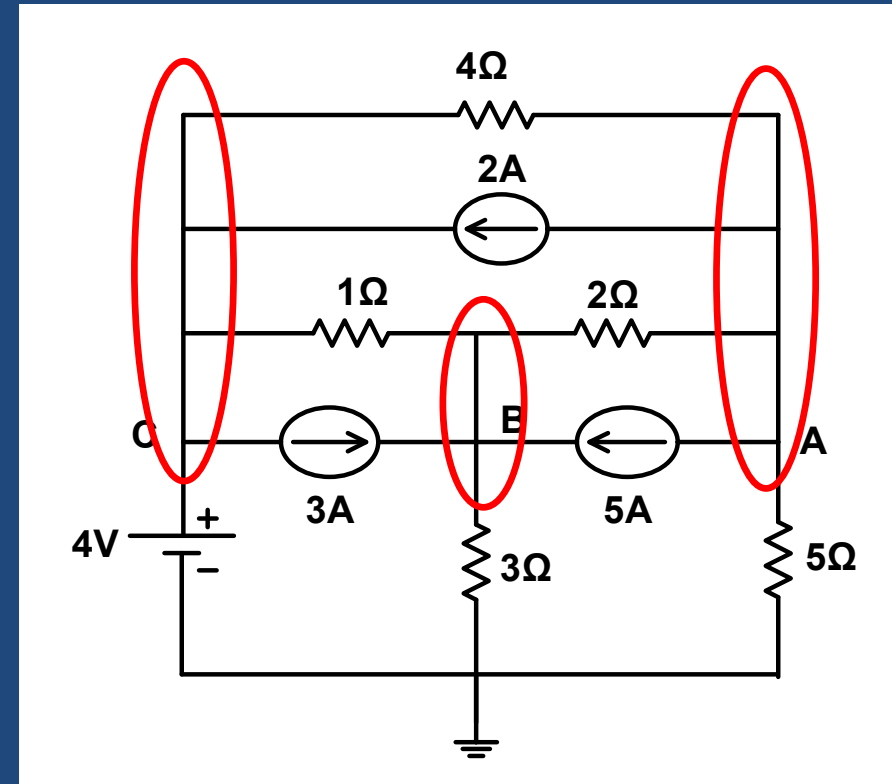

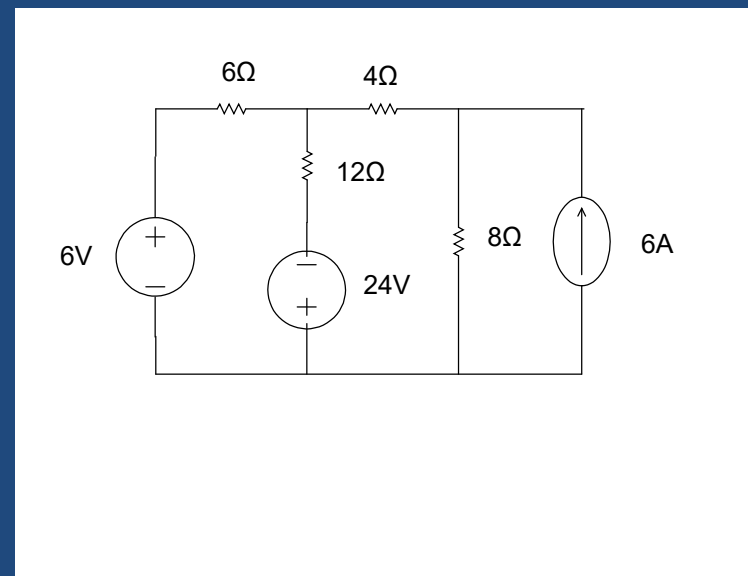Example 6


Calculate voltage V across 8Ω and current I through 12Ω



Solution of example 6

Calculate voltage V across 8Ω and current I through 12Ω


- Identify all nodes
- Ground big node
- $V_A = 6V$
- $V_D = -24V$
- Node B: $-\frac{1}{6}V_A + (\frac{1}{6} + \frac{1}{4} + \frac{1}{12})V_B - \frac{1}{4}V_C - \frac{1}{12}V_D = 0$
- Node C: $-\frac{1}{4}V_B + (\frac{1}{4} + \frac{1}{8})V_C = 6$
- $\Rightarrow V_B = 9V; V_C = 22V = V$
- $I = (V_B - V_D)/12 = [9 - (-24)]/12 = 2.75A$

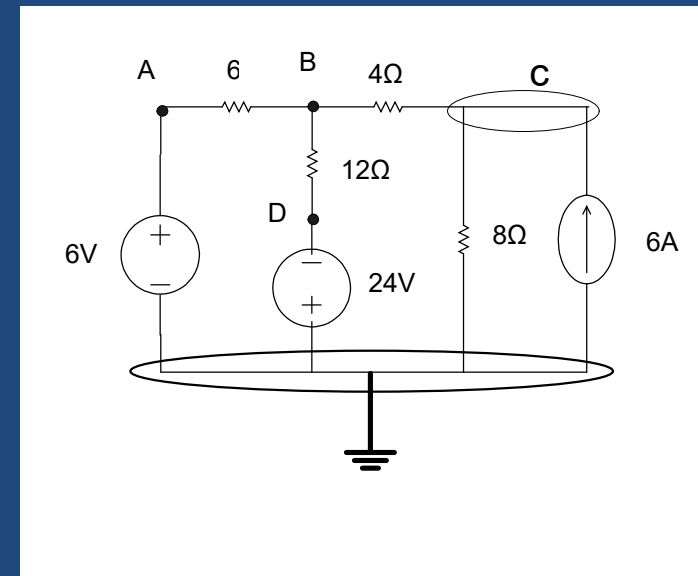

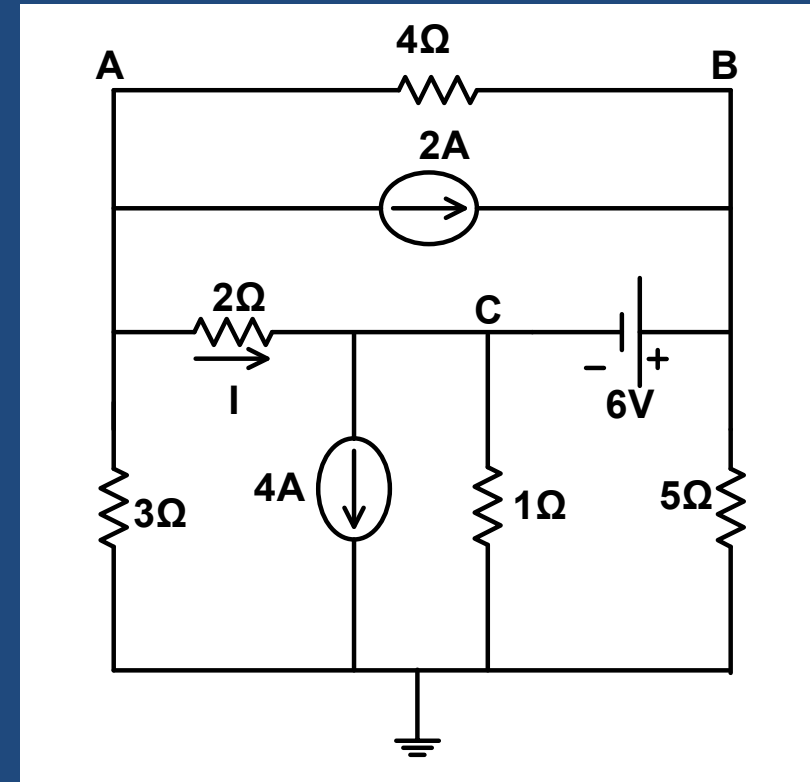Example 7

Determine the voltages V_A and current I

Note: There is a voltage source between 2 nodes => super-node



Solution of example 7

1. Identify all nodes
2. Super-node B and C
3. Equation for each node


$$4. \text{ A: } \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{3}\right) V_A - \frac{1}{4}V_B - \frac{1}{2}V_C = -2 \quad (1)$$

$$5. \text{ B\&C: } -\frac{1}{4} V_A + \left(\frac{1}{4} + \frac{1}{5}\right)V_B + \left(\frac{1}{2} + \frac{1}{1}\right)V_C - \frac{1}{2} V_A = - \quad (2)$$

$$6. \text{ C: } V_B - V_C = 6 \quad (3)$$

$$\Rightarrow V_A = -2.9V; V_B = 2.4V; V_C = -3.6V$$


$$I = (V_A - V_C) / 2 = (-2.9 + 3.6) / 2 = \underline{\underline{0.35A}}$$

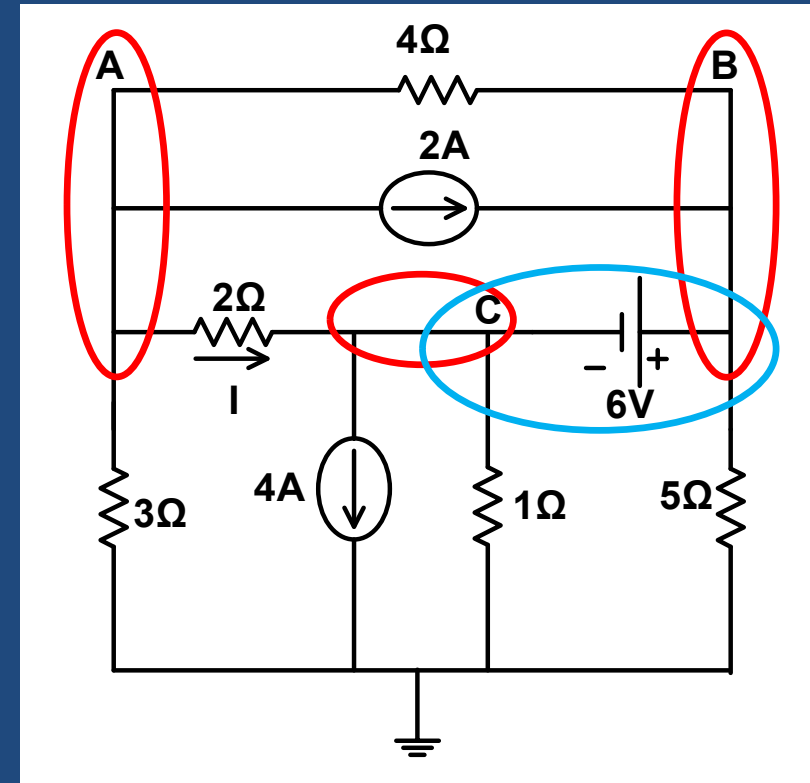

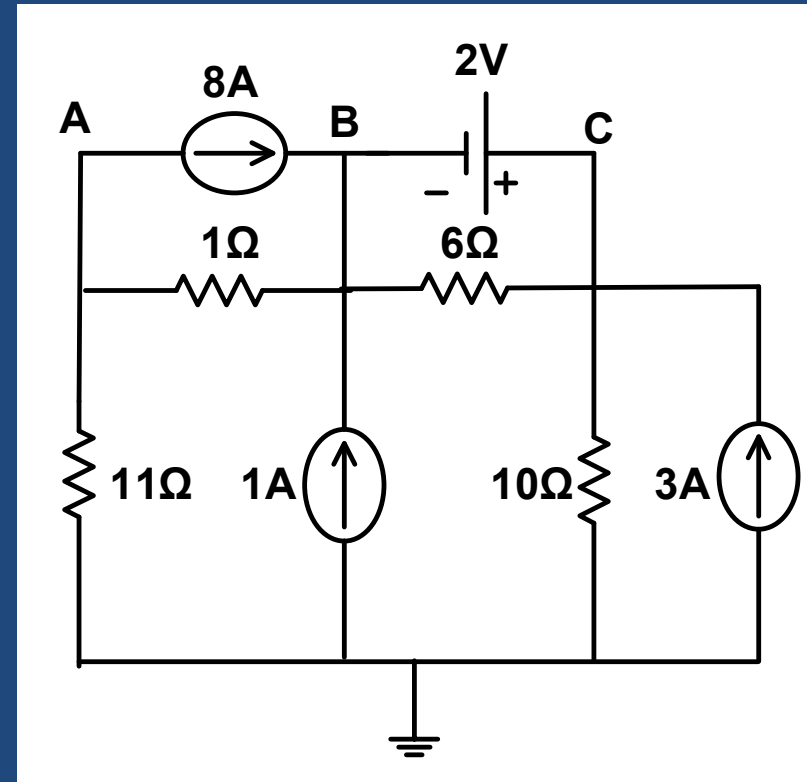Example 8

Determine the voltage V_A

Note: There is a voltage source between 2 nodes => super-node



Solution of example 8

1. Identify all nodes
2. Super-node B and C
3. Equation for each node

$$4. \text{ A: } \left(\frac{1}{1} + \frac{1}{11}\right) V_A - \frac{1}{1} V_B = -8 \quad (1)$$


$$5. \text{ B \& C: } -\frac{1}{1} V_A + \frac{1}{1} V_B + \frac{1}{10} V_C = 1 + 8 + 3 \quad (2)$$

$$6. \text{ C: } V_C - V_B = 2 \quad (3)$$

$$\Rightarrow V_A = \underline{15V}$$

Note: Why did we ignore 6Ω in (2)?
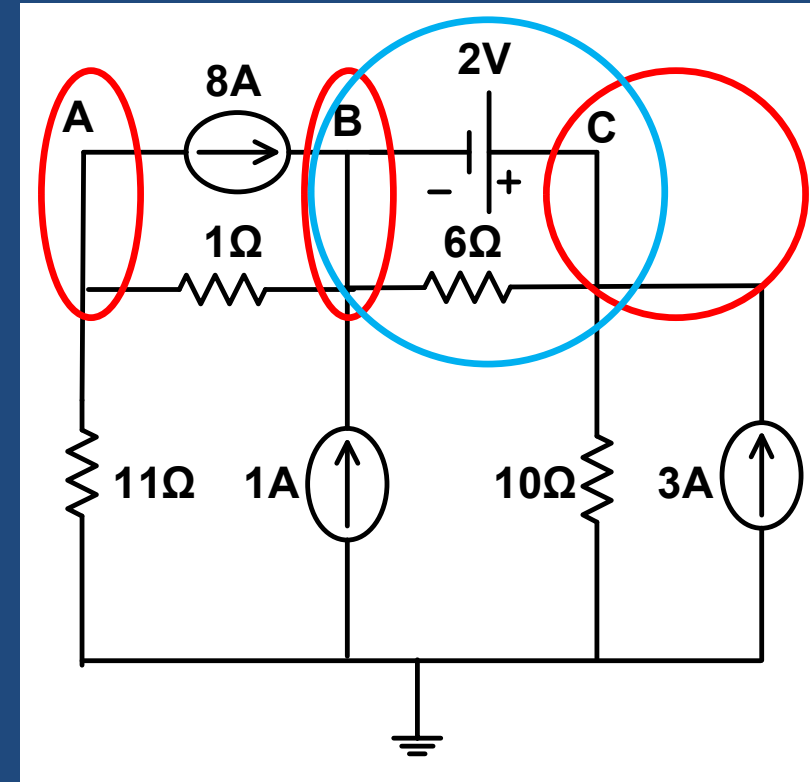
$$\begin{aligned} \text{B \& C: } & -\frac{1}{1} V_A + \left(\frac{1}{1} + \frac{1}{6}\right) V_B - \frac{1}{6} V_C + \left(\frac{1}{10} + \frac{1}{6}\right) V_C - \frac{1}{6} V_B = 1 + 8 + 3 \\ & -\frac{1}{1} V_A + \left(\frac{1}{1}\right) V_B + \frac{1}{10} V_C = 1 + 8 + 3 \quad (2) \end{aligned}$$




3. SOURCE CONVERSION (TRANSFORMATION) METHOD

Method


- a) Thevenin form (with E and R in series) \Rightarrow Norton form: $I = E/R$ and R in parallel
- b) Norton form (with I and R in parallel) \Rightarrow Thevenin form: $E = IR$ and R in series

Warning: do not converse the question


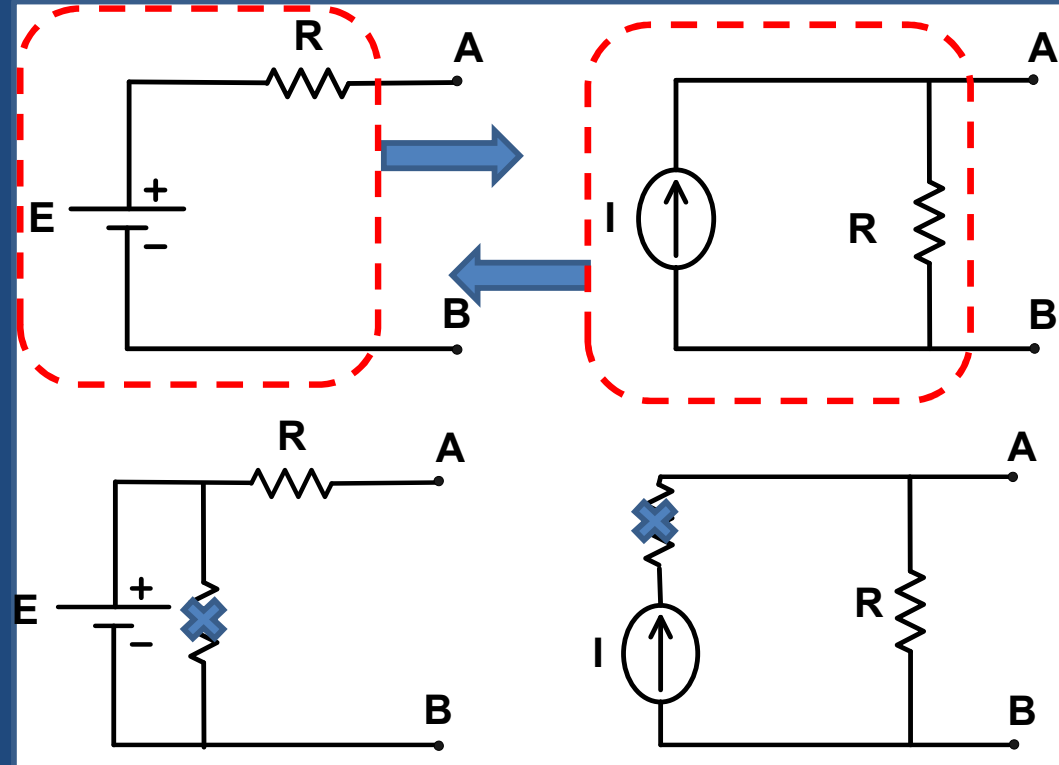


Example 9


Determine the current I

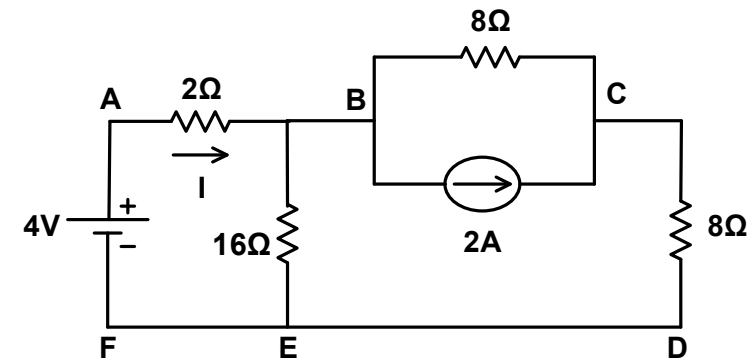









Solution of example 9

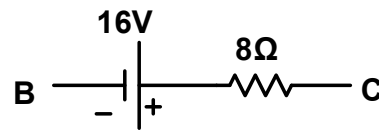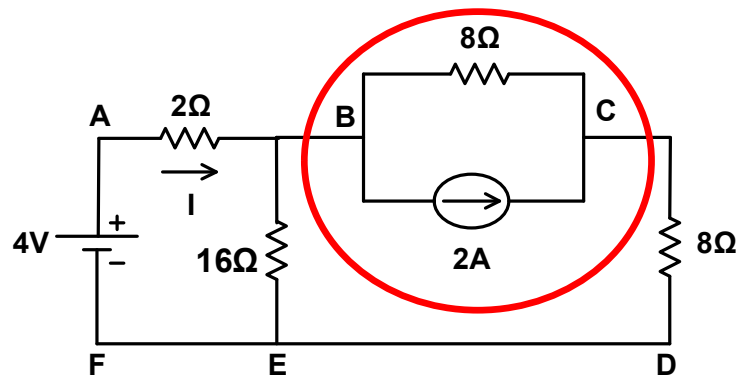

Solution of example 9 (cont.)

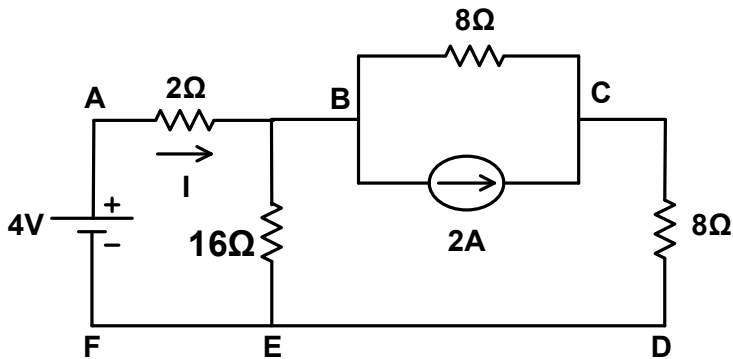


$$I = (4 + 8) / (2 + 8) = 1.2A$$

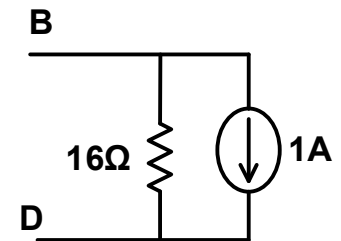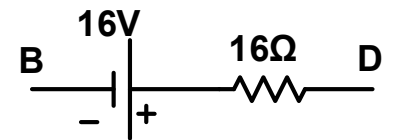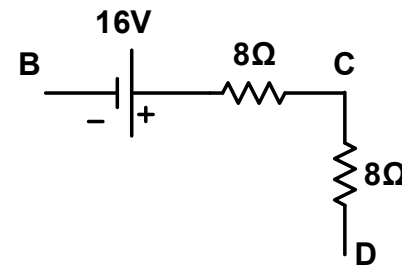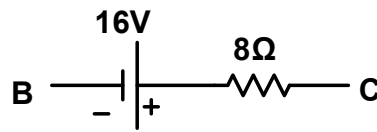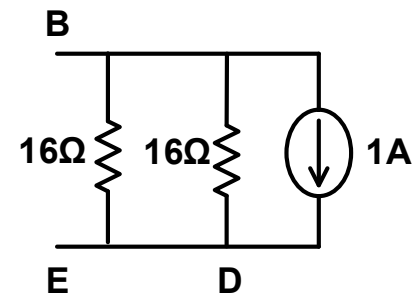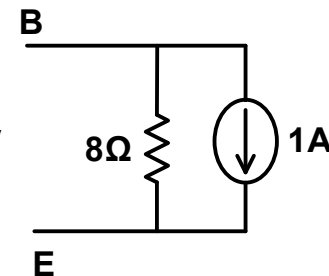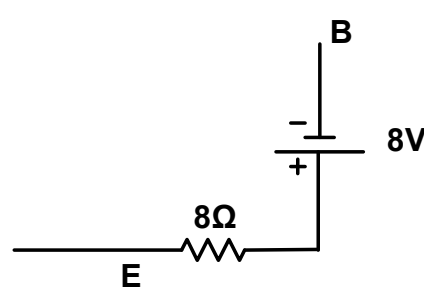
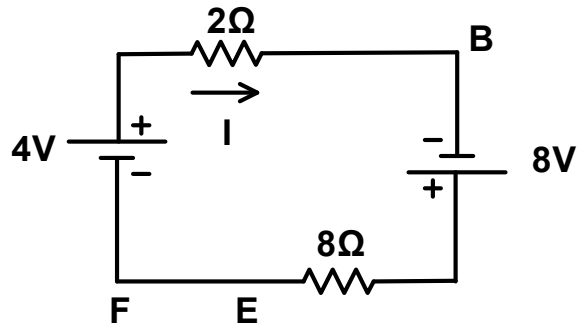


Example 10



Determine the voltage V

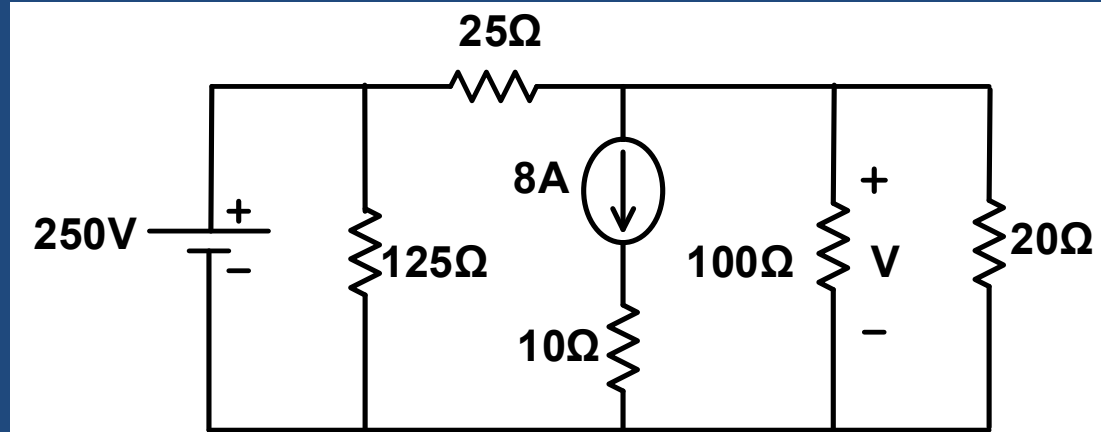

Solution of example 10

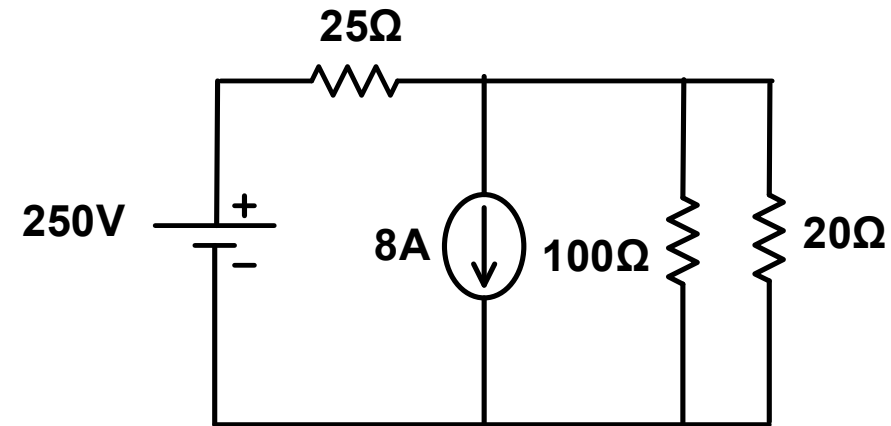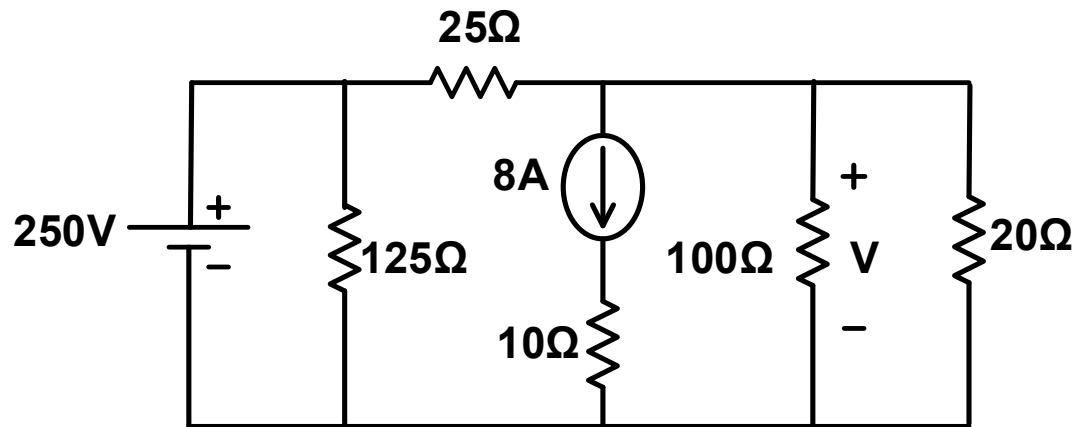

$$V = 2 \times 10 = 20V$$

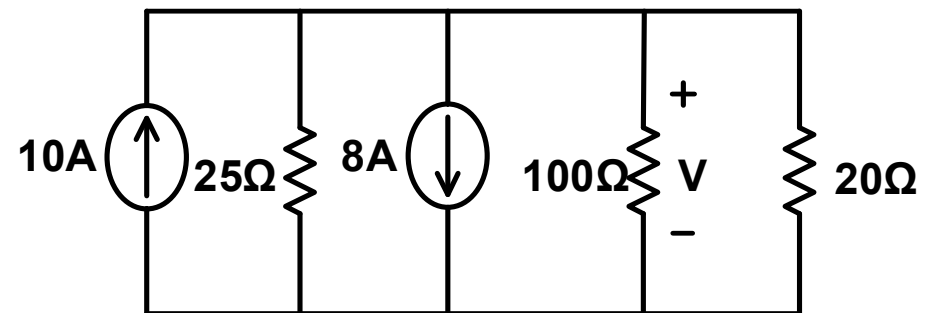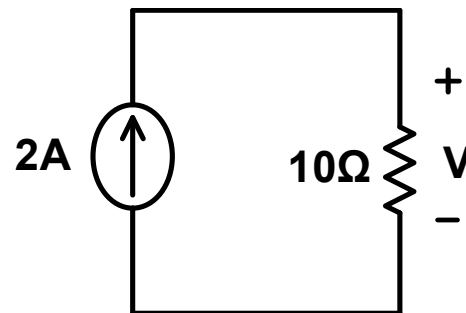

4. SUPERPOSITION METHOD

Principle

The superposition principle: For all linear systems, the net response caused by two or more stimuli is the sum of the responses that would have been caused by each stimulus individually => to test the linearity of a function.

Test the linearity

Is function $Y = 2X$ linear?

$$X_1 = 1 \Rightarrow Y_1 = 2$$

$$X_2 = 2 \Rightarrow Y_2 = 4$$

$$\text{If } X_3 = X_1 + X_2 = 3$$

$$\text{Is } Y_3 = Y_1 + Y_2 \text{ i.e., } Y_3 = 2 + 4 = 6?$$

$$\text{Test: } X_3 = 3 \Rightarrow Y_3 = 6$$

Conclusion: This function is linear

Is $Y = 2X^2$ linear?

$$X_1 = 1 \Rightarrow Y_1 = 2$$

$$X_2 = 2 \Rightarrow Y_2 = 8$$

$$X_3 = X_1 + X_2 = 3$$

$$\text{Is } Y_3 = Y_1 + Y_2 \text{ i.e., } Y_3 = 2 + 8 = 10?$$

$$\text{Test: } X_3 = 3 \Rightarrow Y_3 = 18$$

Conclusion: This function is nonlinear


Superposition theorem

In an electrical circuit with many sources, the voltage or current is equal to the algebraic sum of the responses caused by each independent source acting alone.


Method

1. Keep one source, kill other voltage and current sources

Kill voltage
source

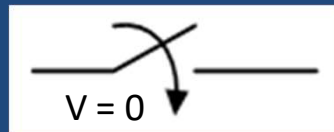


Kill current
source

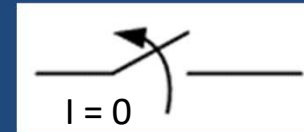

2. Calculate voltage or current due to the one remained source
3. Repeat the same with another source until the last source
4. Sum the results.


Warning: Apply to calculate only V or I ($V = RI$) but not $P = RI^2$

Example 11: Find I

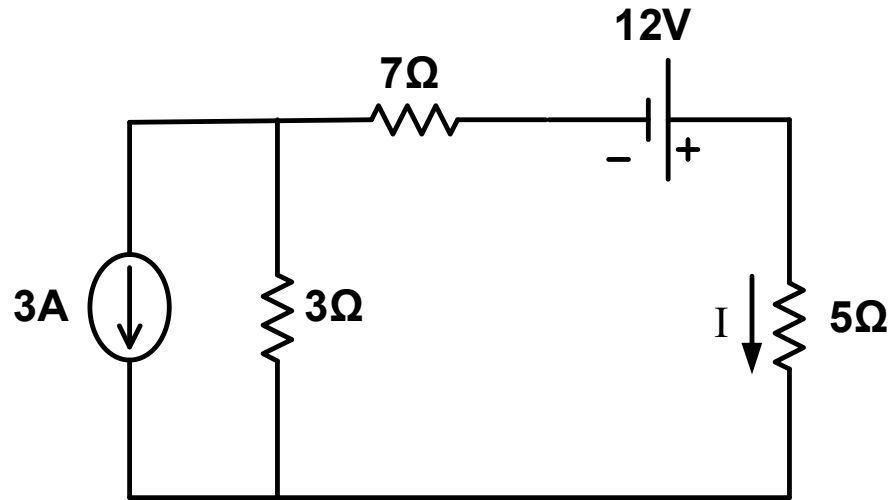


$$I = I_{12} + I_3$$

$$= 0.8 - 0.6 = \underline{\underline{0.2A}}$$

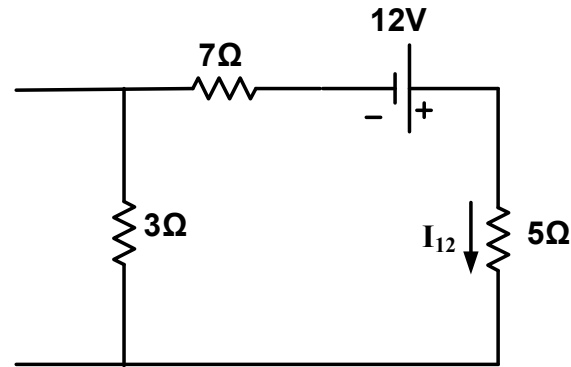

Keep 12V
Kill 3A \Rightarrow OC

$$I_{12} = \frac{12}{7 + 3 + 5} = 0.8A$$

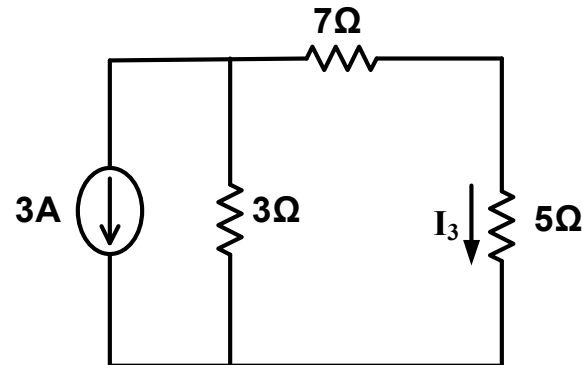


Keep 3A
Kill 12V \Rightarrow SC


$$I_3 = -3 \frac{3}{7 + 3 + 5} = -0.6A$$

Example 12

Determine the current I

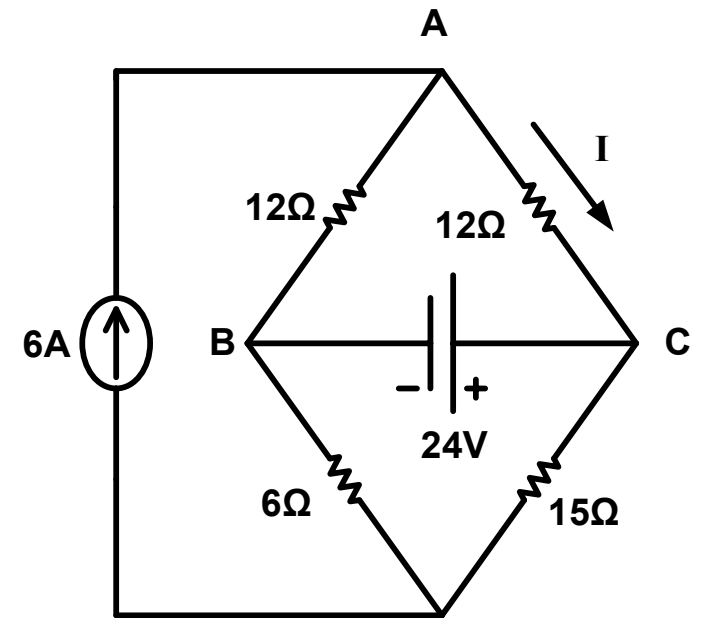


Solution of example 12

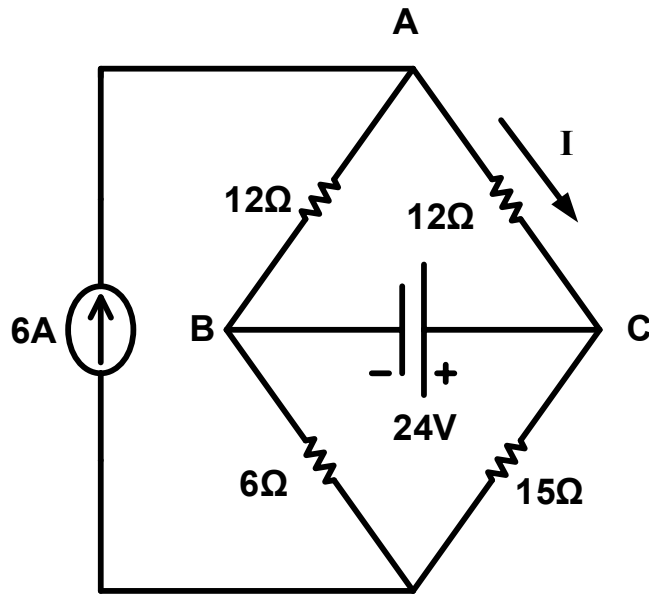


$$I = I_6 + I_{24}$$

$$= 3 - 1 = 2A$$

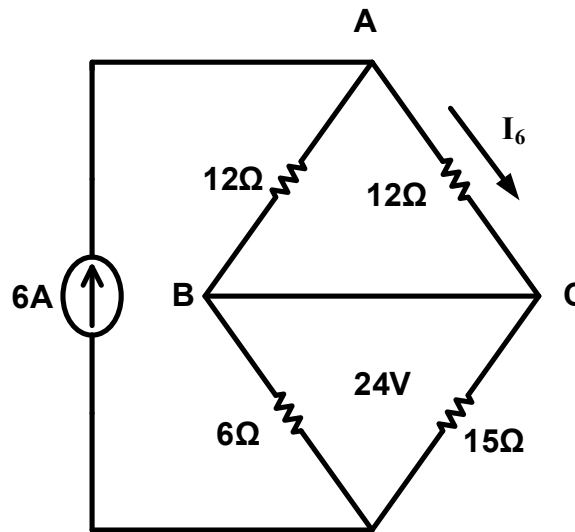


Keep 6A
Kill 24V \Rightarrow SC
Current divider:
 $I_6 = 3A$

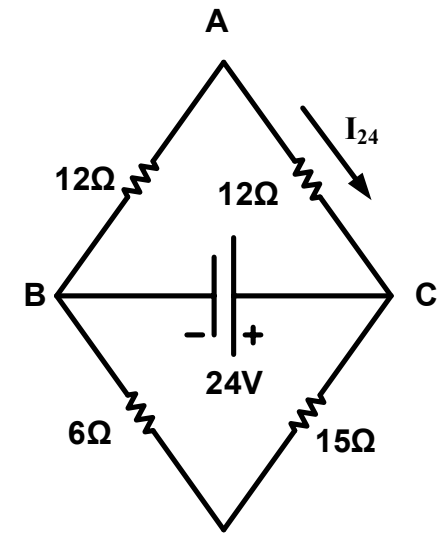


Keep 24V
Kill 6A \Rightarrow OC
Ohm's law
 $I_{24} = -24/(12+12) = -1A$

Solution of example 12 (cont.)

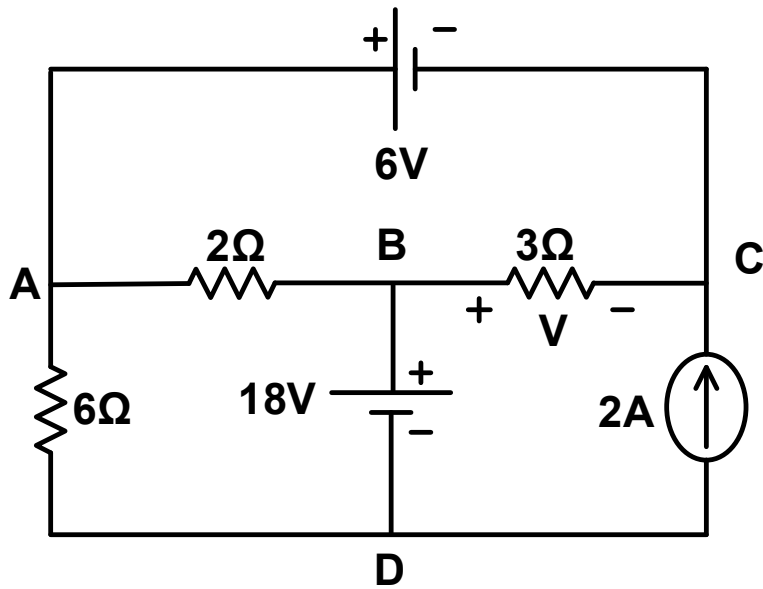

$$V = V_6 + V_{18} + V_2$$

$$= 4$$

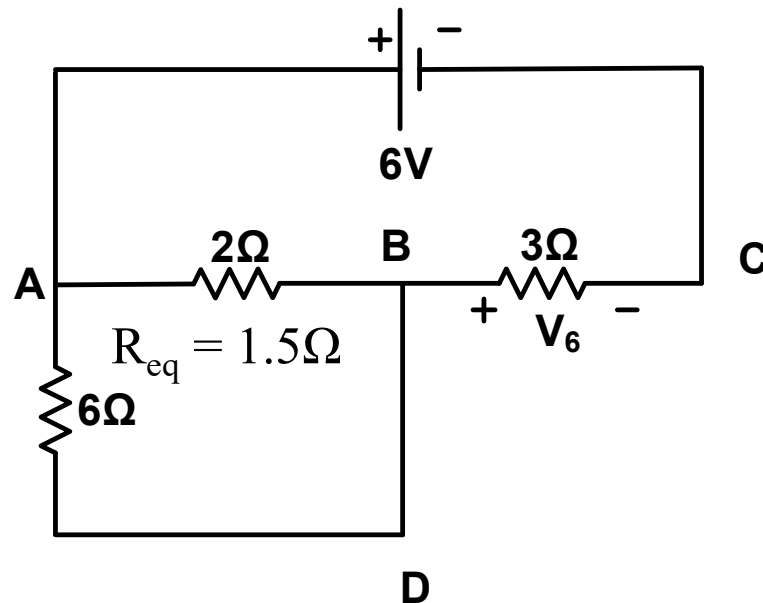


Keep 6V

Kill 2A \Rightarrow OC; kill 18V \Rightarrow SC


Voltage divider $V_6 = 6 \frac{3}{3 + 1.5} = 4V$

Solution of example 12 (cont.)

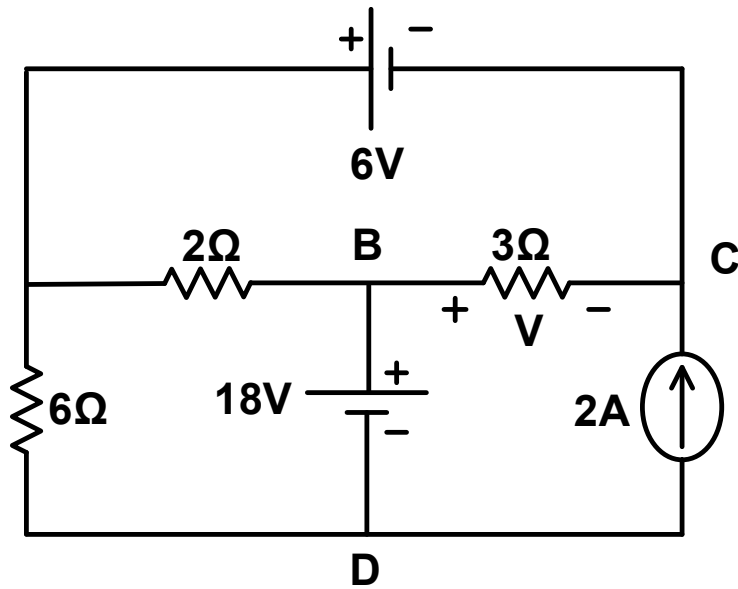


$$V = V_6 + V_{18} + V_2$$

$$= 4 + 3$$

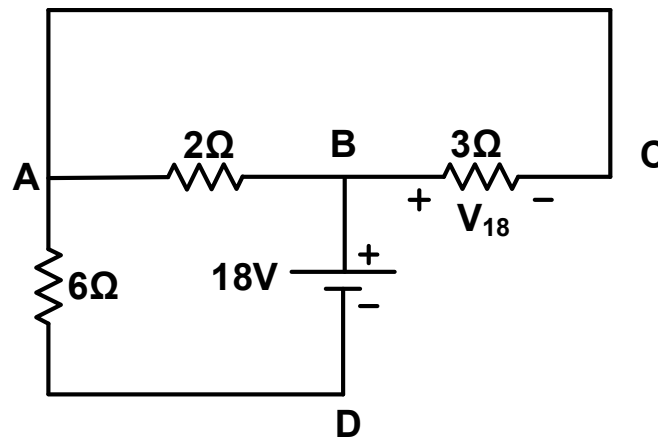


Keep 18V
Kill 2A \Rightarrow OC; kill 6V \Rightarrow SC
Voltage divider:
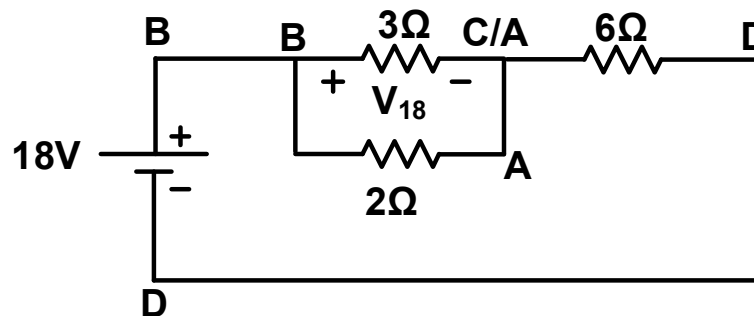
$$V_{18} = 18 \frac{6/5}{(6/5) + 6} = 3V$$





Solution of example 12 (cont.)

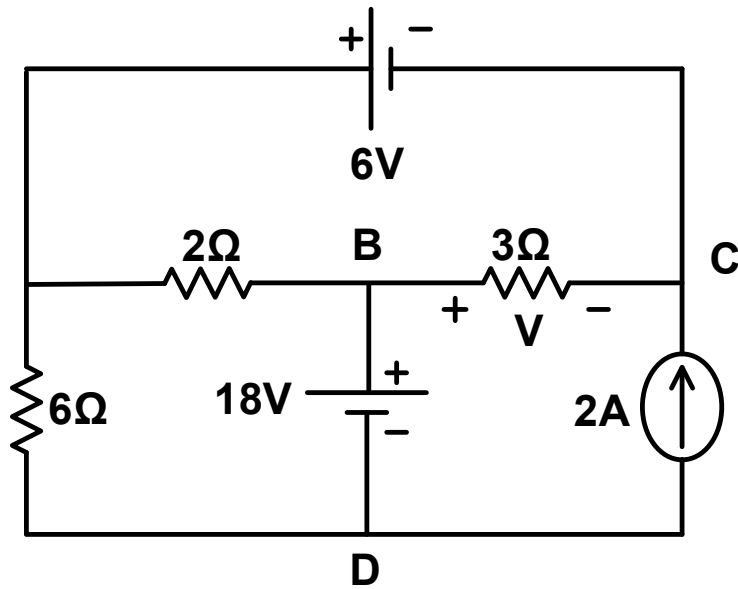

$$V = V_6 + V_{18} + V_2$$


$$= 4 + 3 - 2 = \underline{\underline{5V}}$$

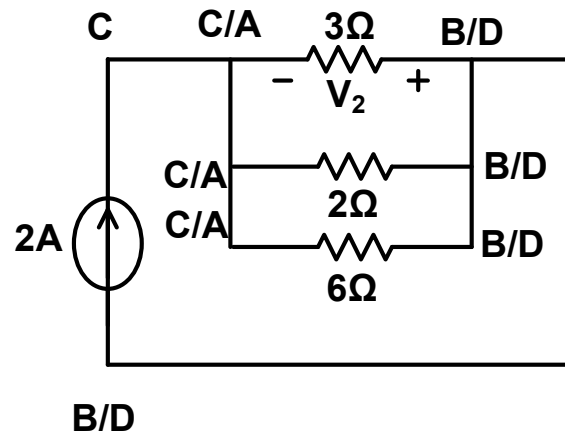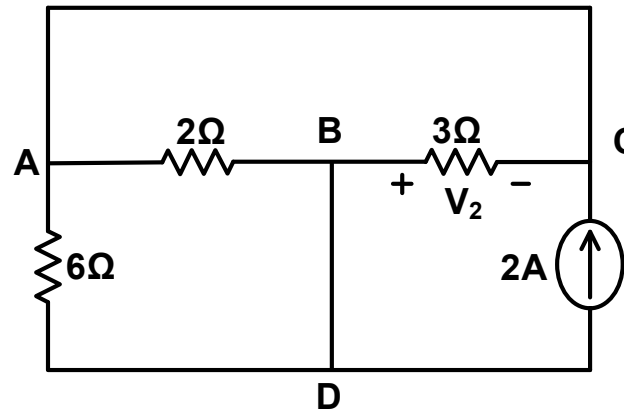

Keep 2A
Kill 6V \Rightarrow SC; kill 18V \Rightarrow SC
 $R_{eq} = 1\Omega$
 $V_2 = -2 \times 1 = -2V$

Example 13

Determine the currents I_1 , I_2 and I_3

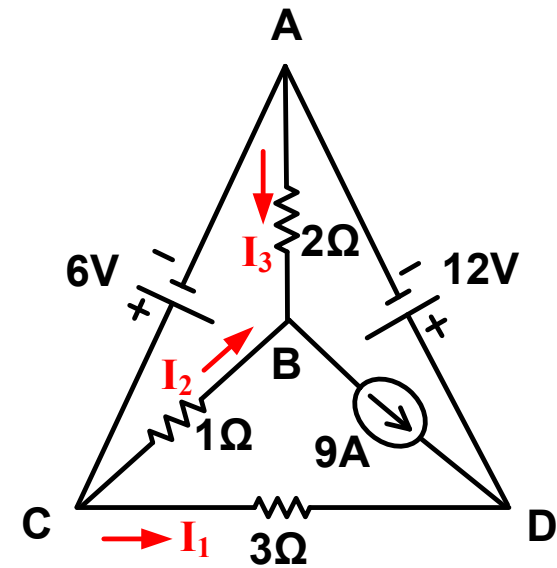


Solution of example 13

$$I_1 = I_{1.6} + I_{1.12} + I_{1.9}$$

$$I_2 = I_{2.6} + I_{2.12} + I_{2.9}$$

$$I_3 = I_{3.6} + I_{3.12} + I_{3.9}$$

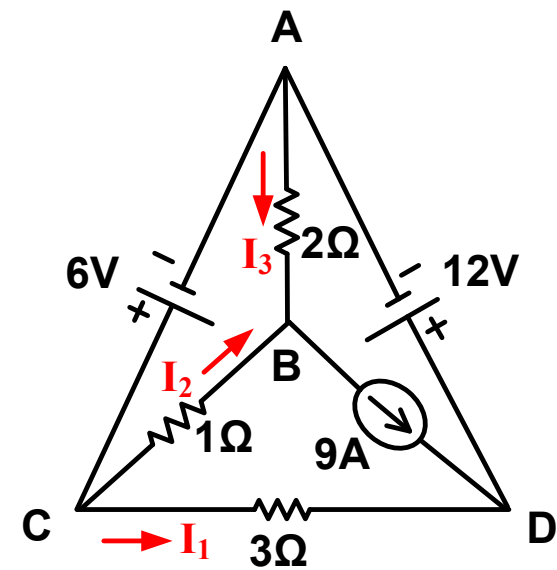


Solution of example 13 (cont.)

$$I_1 = I_{1.6} + I_{1.12} + I_{1.9} \\ = 2 + \dots$$

$$I_2 = I_{2.6} + I_{2.12} + I_{2.9} \\ = 2 + \dots$$
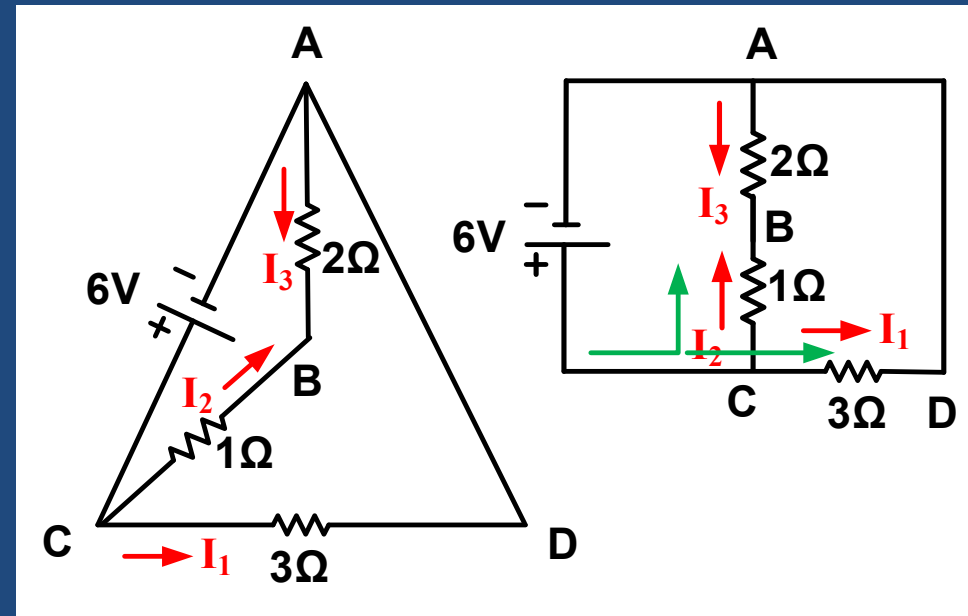
$$I_3 = I_{3.6} + I_{3.12} + I_{3.9} \\ = -2 + \dots$$




Solution of example 13 (cont.)

$$\begin{aligned} I_1 &= I_{1.6} + I_{1.12} + I_{1.9} \\ &= 2 - 4 + \dots \end{aligned}$$

$$\begin{aligned} I_2 &= I_{2.6} + I_{2.12} + I_{2.9} \\ &= 2 + 0 + \dots \end{aligned}$$
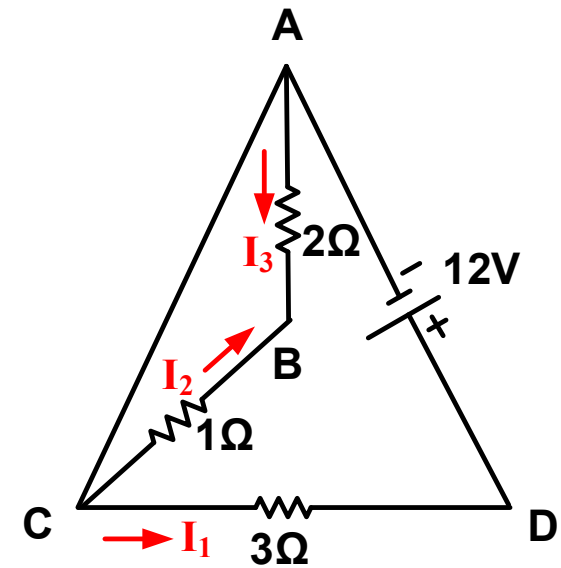
$$\begin{aligned} I_3 &= I_{3.6} + I_{3.12} + I_{3.9} \\ &= -2 + 0 + \dots \end{aligned}$$




Solution of example 13 (cont.)

$$\begin{aligned} I_1 &= I_{1.6} + I_{1.12} + I_{1.9} \\ &= 2 - 4 + 0 = -2A \end{aligned}$$


$$\begin{aligned} I_2 &= I_{2.6} + I_{2.12} + I_{2.9} \\ &= 2 + 0 + 6 = 8A \end{aligned}$$
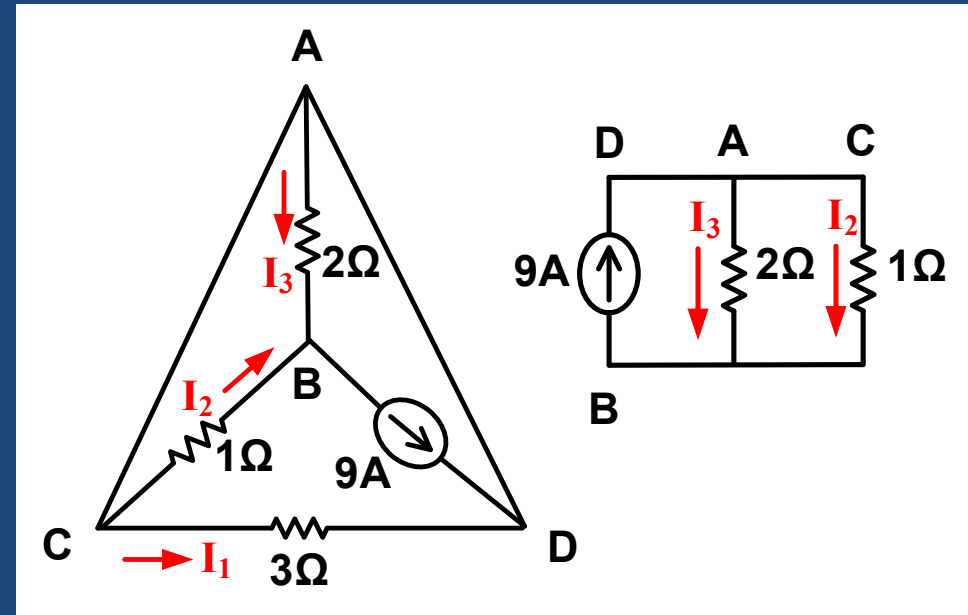
$$\begin{aligned} I_3 &= I_{3.6} + I_{3.12} + I_{3.9} \\ &= -2 + 0 + 3 = 1A \end{aligned}$$



5. THEVENIN AND NORTON METHODS

Concept of networks

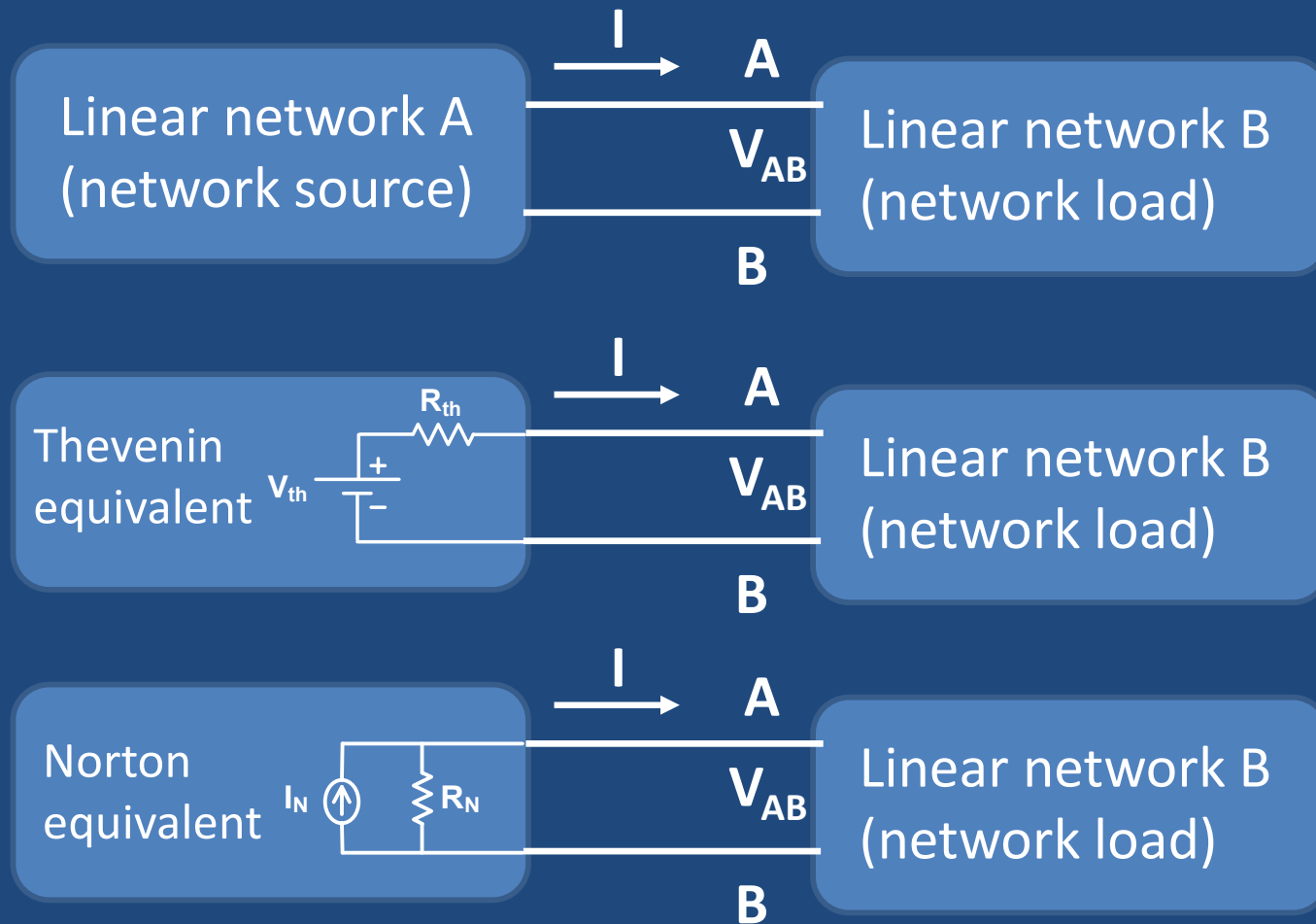


Thevenin equivalent circuit

Statement:





1. $V_{th} = V_{AB|oc}$
2. R_{th} = Resistance of the dead network

Method:

1. Remove the load
2. Kill all sources then calculate R_{eq} looked from A and B $\Rightarrow R_{th}$
3. Put back all sources then calculate $V_{AB|oc} \Rightarrow V_{th}$

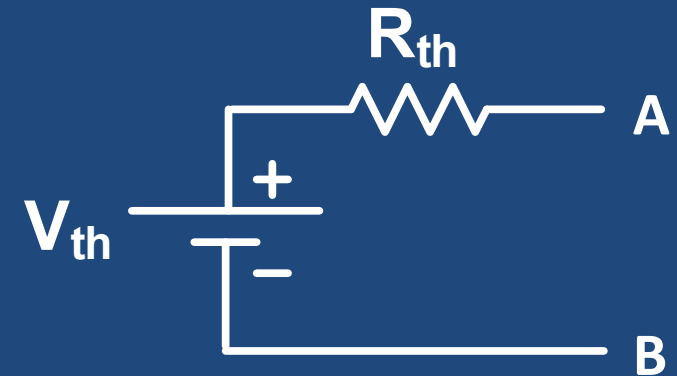


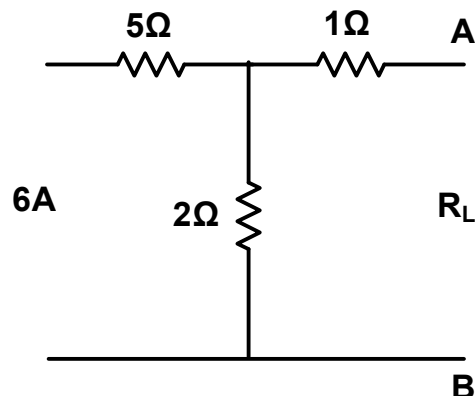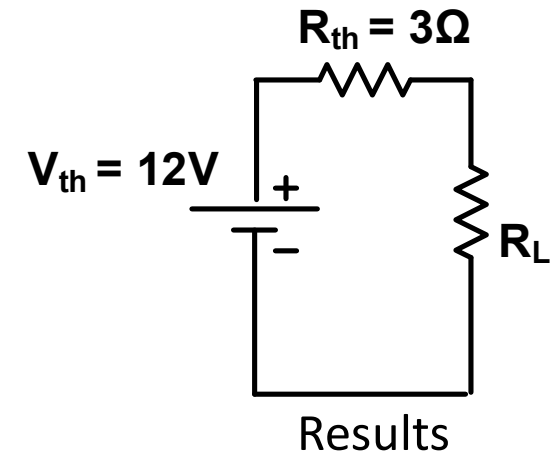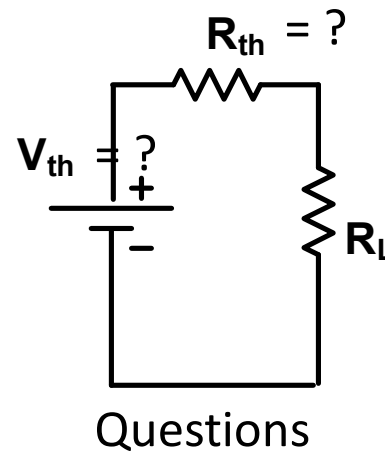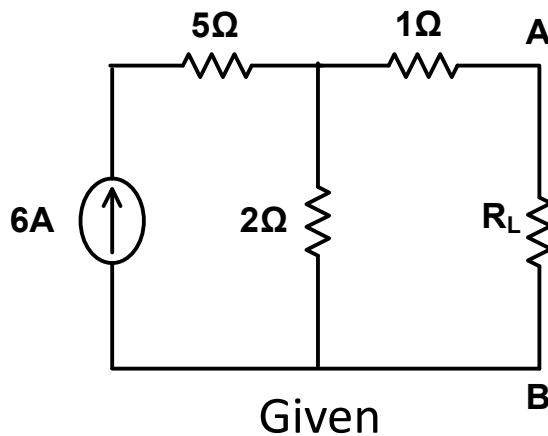Example 14: Determine the Thevenin equivalent circuit




Remove the load and kill the source:

$$R_{th} = R_{AB|OC} = 3\Omega$$

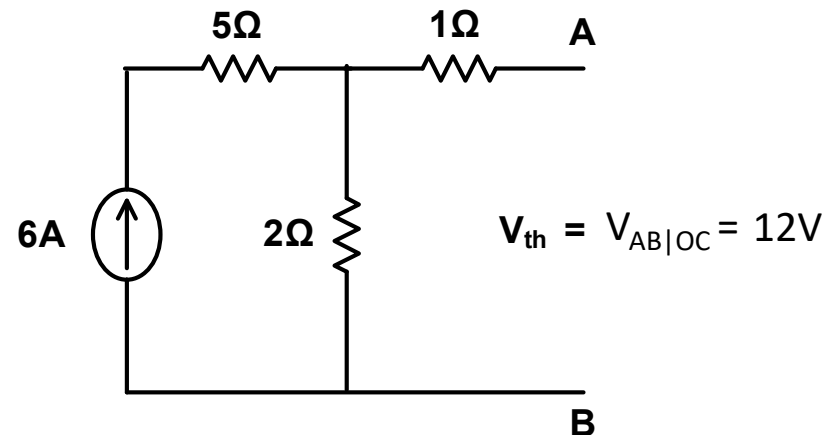


Example 15




Determine the current I

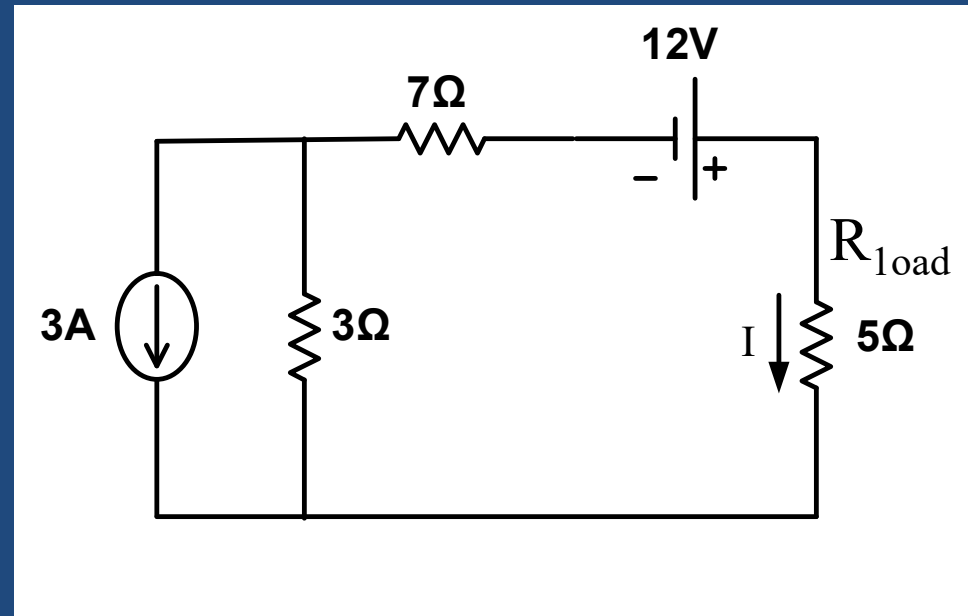

Solution of example 15

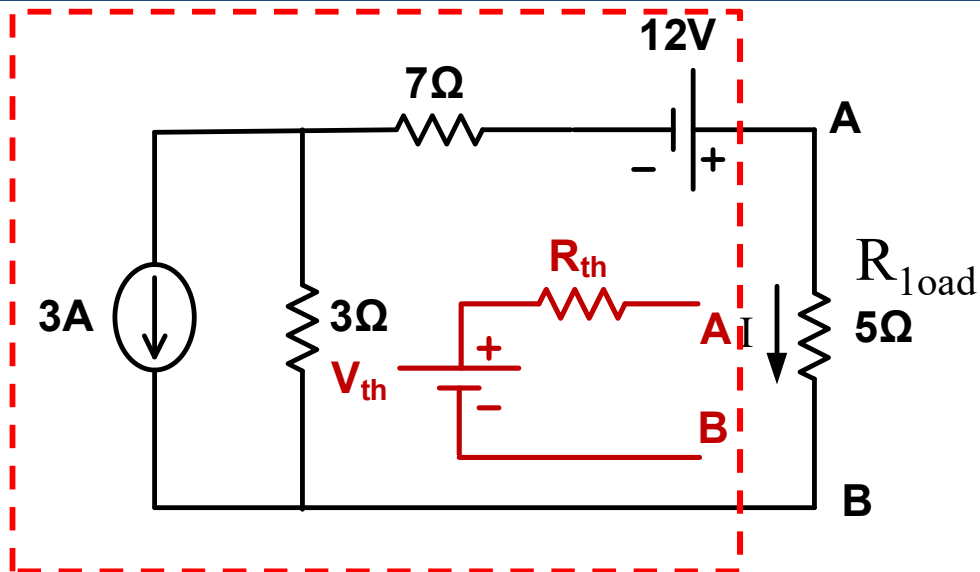
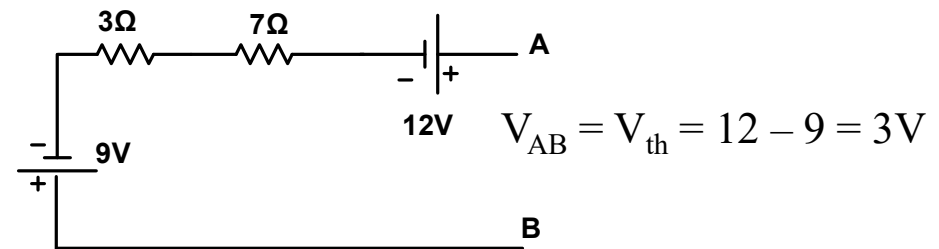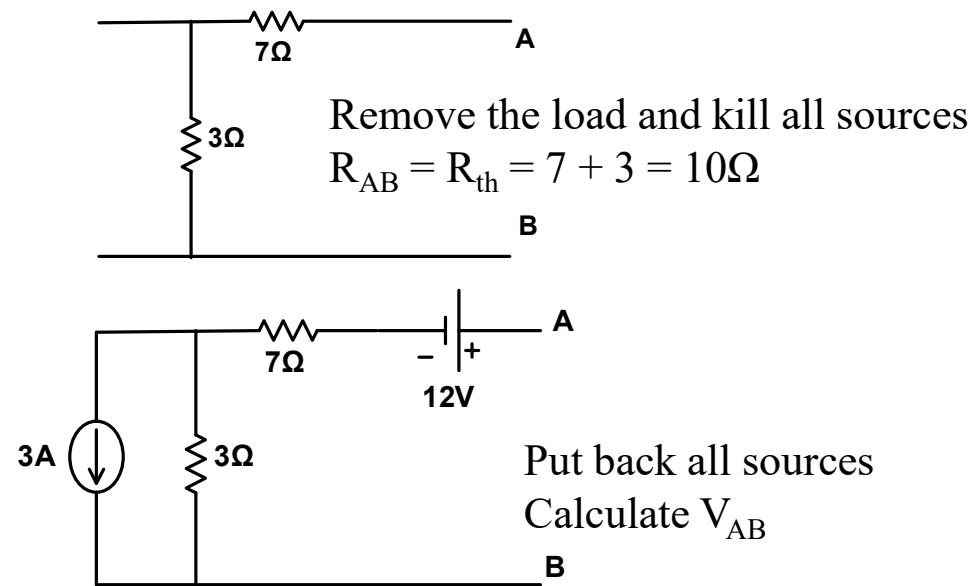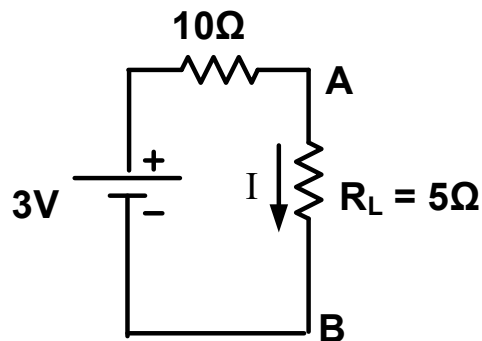
$$I = \frac{3}{10+5} = \underline{\underline{0.2A}}$$




Norton equivalent circuit

Statement:





1. R_N = Resistance of the dead network
2. $I_N = I_{AB|sc}$

Method:

1. Remove the load
2. Kill all sources then calculate R_{eq} looked from A and B $\Rightarrow R_N$
3. Put back all sources, short circuit AB then calculate $I_{AB|sc} \Rightarrow I_N$

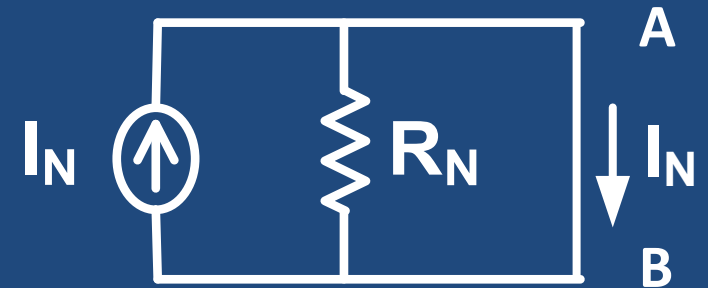


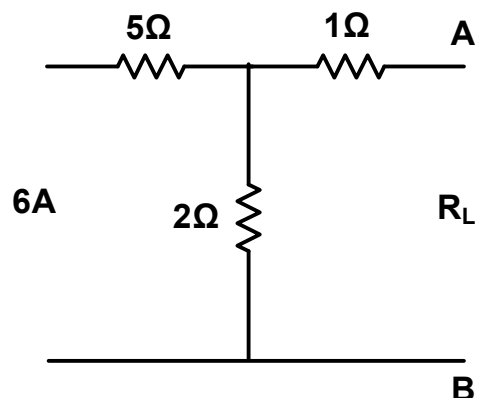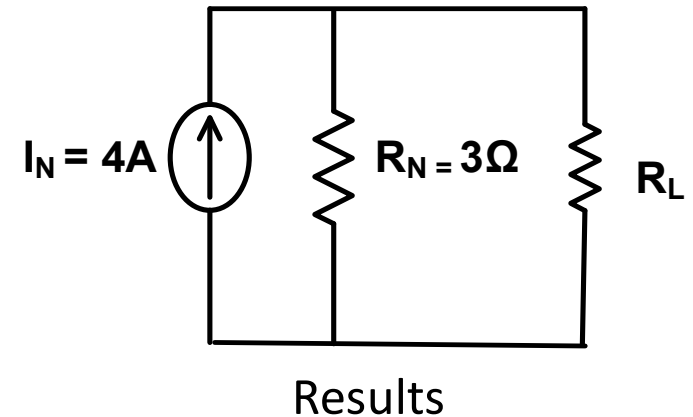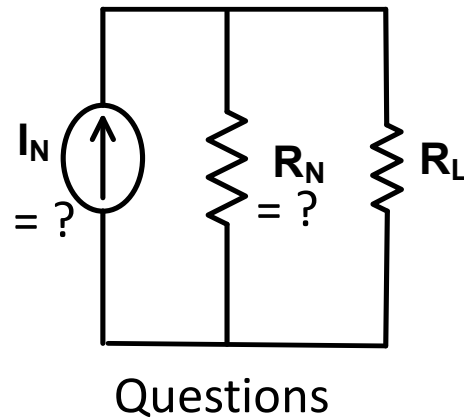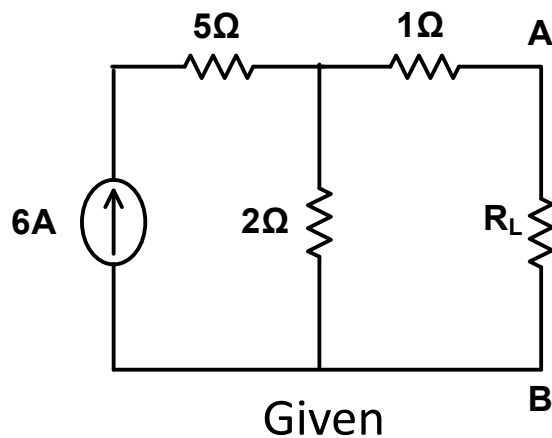Example 16: Determine the Norton equivalent circuit




Remove the load and kill the source:

$$R_{th} = R_{AB|OC} = 3\Omega$$


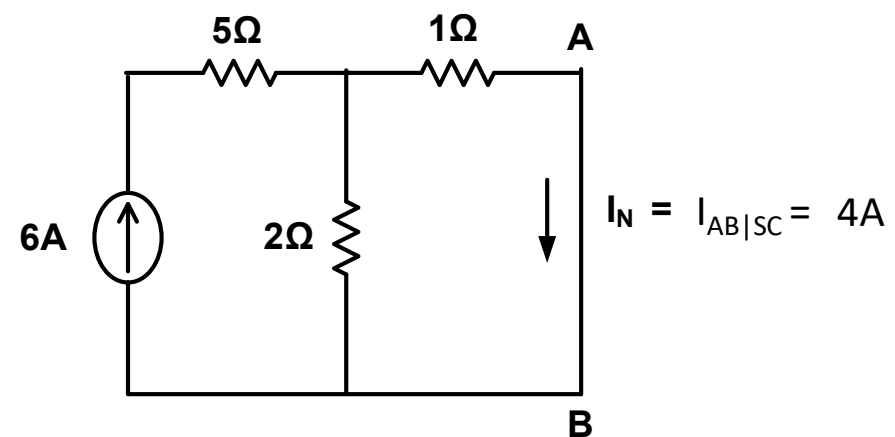


Example 17


Determine the current I

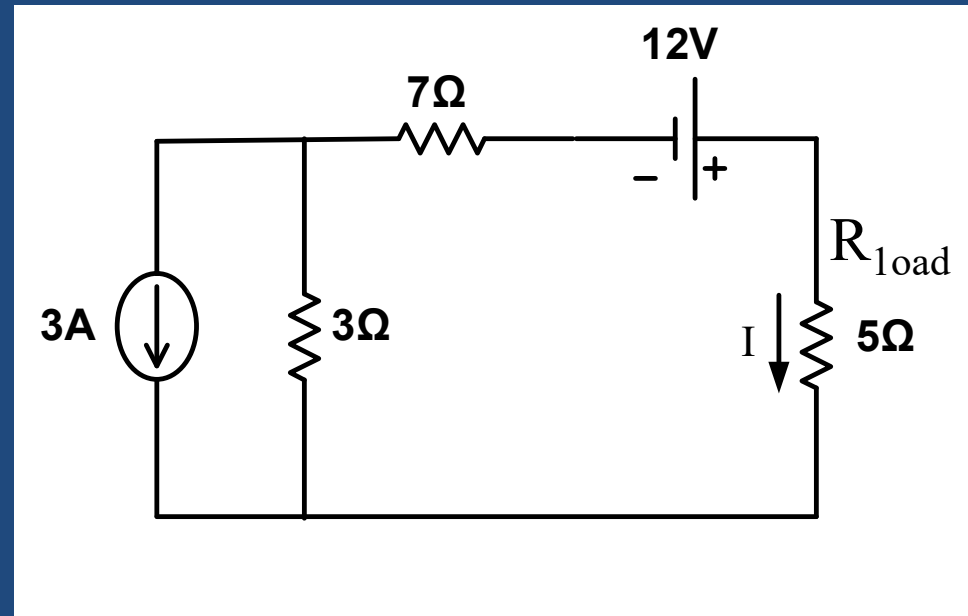


Solution of example 17

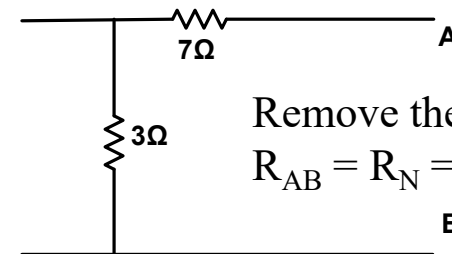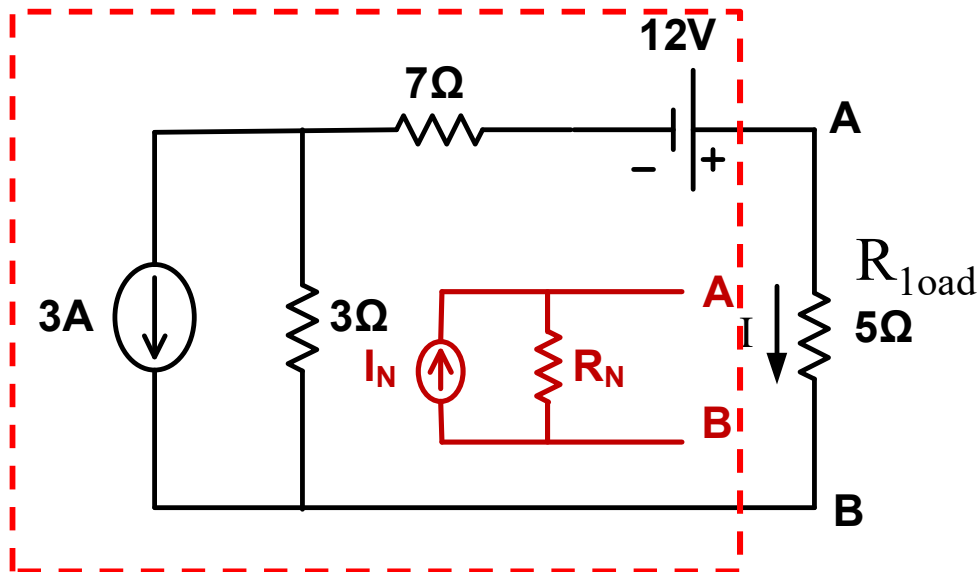

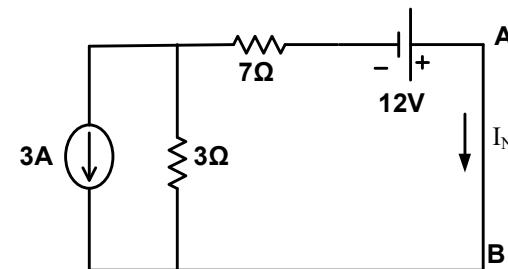
Remove the load and kill all sources
 $R_{AB} = R_N = 7 + 3 = 10\Omega$



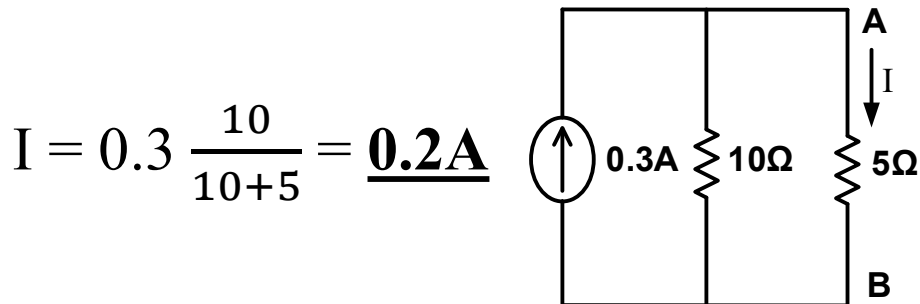Put back all sources
 SC AB
 Calculate I_{AB}



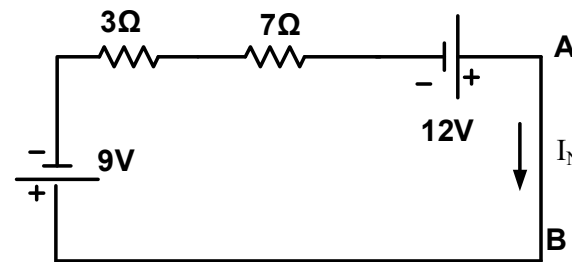
$$I = 0.3 \frac{10}{10+5} = \underline{\underline{0.2A}}$$





$$I_{AB} = I_N = \frac{12 - 9}{3 + 7} = 0.3A$$

Example 18

Determine the current I

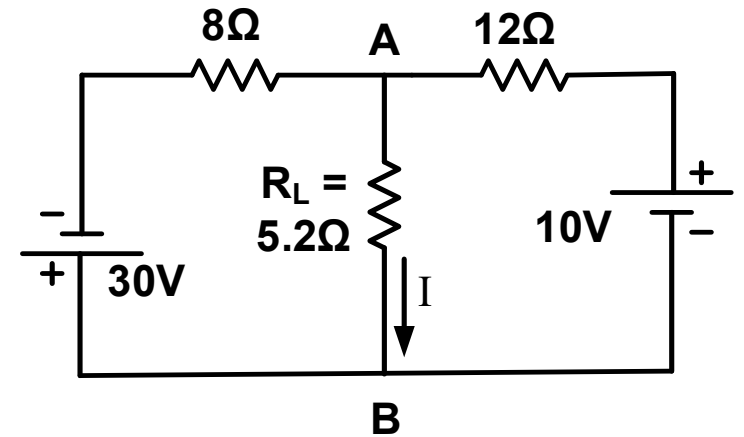

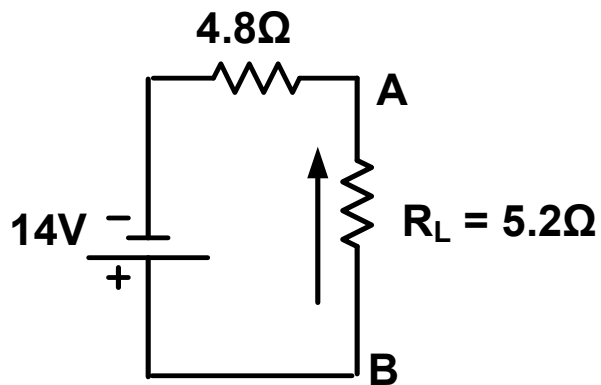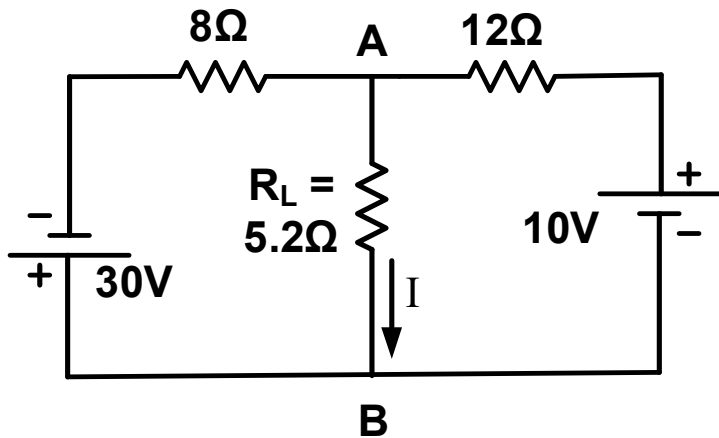Solution of example 18: Thevenin equivalent



Calculate R_{th}

$$R_{th} = \frac{8 \cdot 12}{8 + 12} = 4.8\Omega$$



Calculate V_{th}

$$V_{th} = V_{AB} = V_{AC} + V_{CB}$$


$$V_{AC} = \frac{30}{8 + 12} \cdot 8 = 16V$$

$$V_{th} = V_{AB} = 16 - 30 = -14V$$
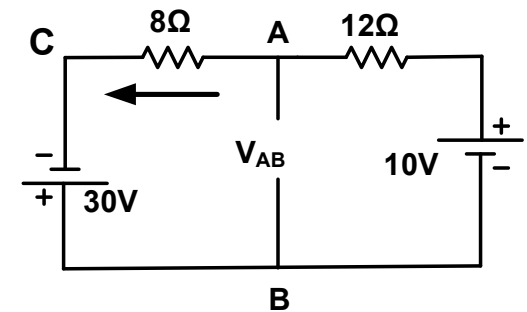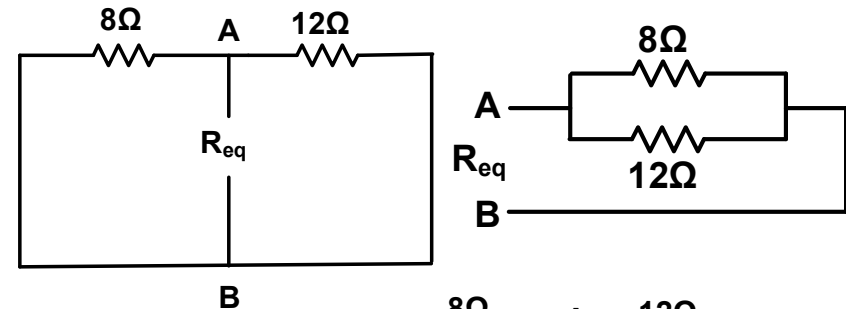
$$I = \frac{-14}{4.8 + 5.2} = -\underline{1.4A}$$




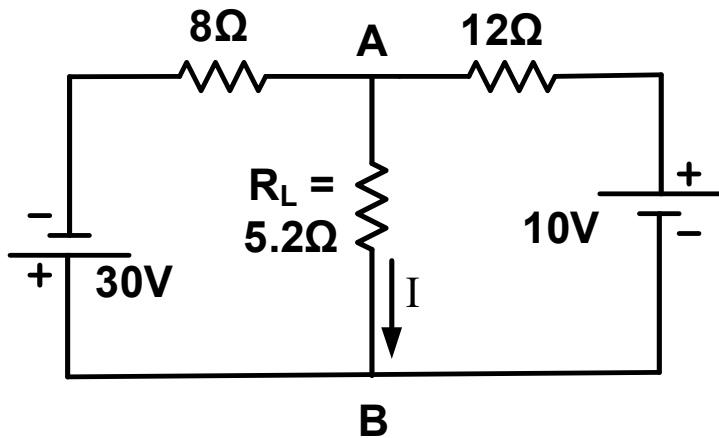
Solution of example 18: Norton equivalent



$$R_N = R_{th} = 4.8\Omega$$

Calculate I_N

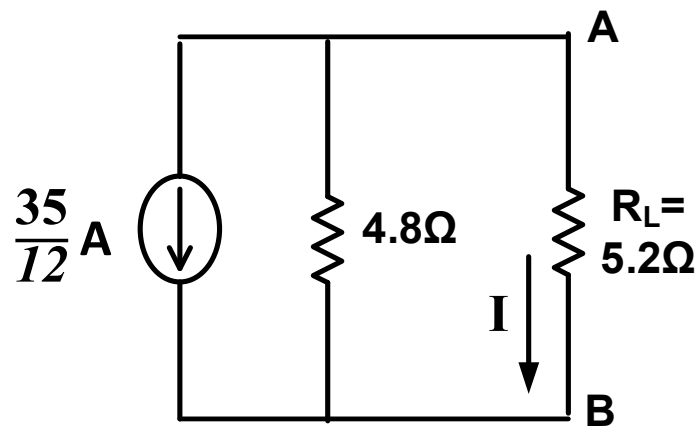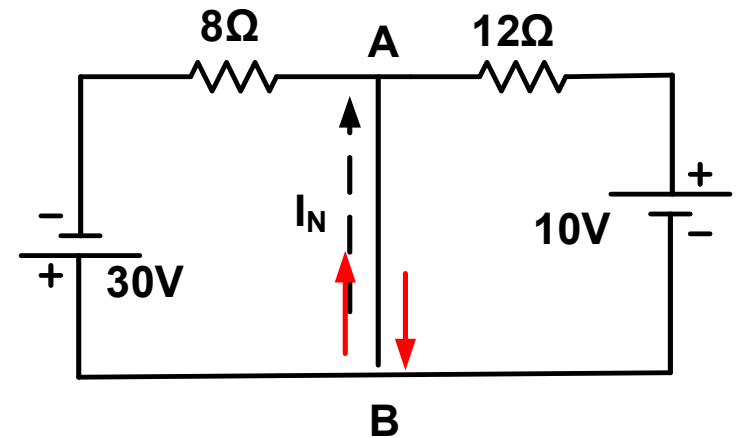
$$I_N = \frac{30}{8} - \frac{10}{12} = \frac{35}{12} \text{ A}$$



$$I = -\frac{35}{12} \frac{4.8}{4.8 + 5.2} = -1.4 \text{ A}$$

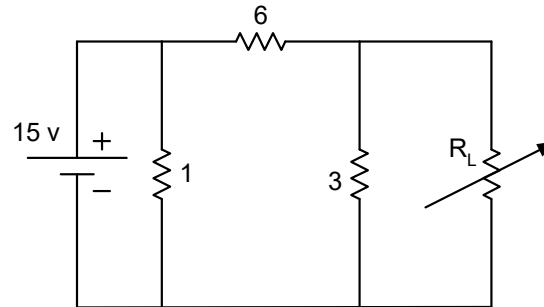
Example 19:

Find the Thevenin equivalent circuits of the following ones




$$\text{Ans: } R_{th} = 2\Omega$$

$$V_{th} = 5V$$

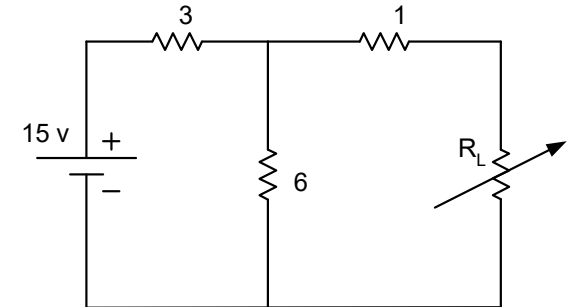


$$\text{Ans: } R_{th} = 3\Omega$$

$$V_{th} = 10V$$

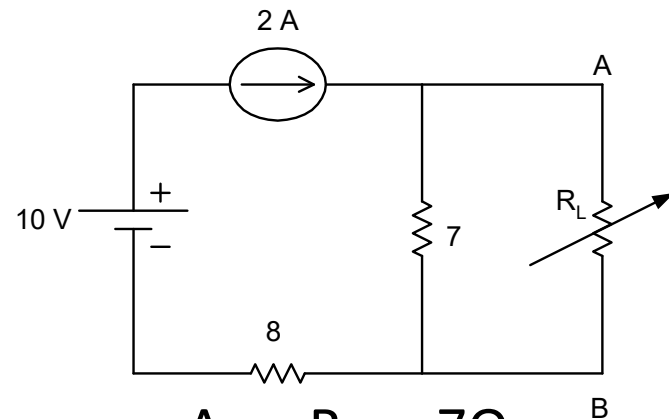


$$\text{Ans: } R_{th} = 7\Omega$$

$$V_{th} = 14V$$

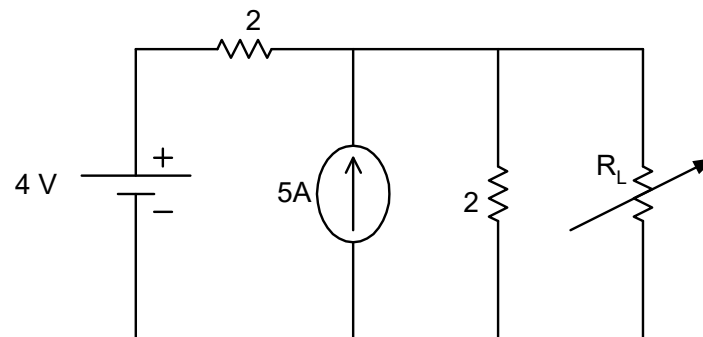

$$\text{Ans: } R_{th} = 1\Omega$$

$$V_{th} = 7V$$

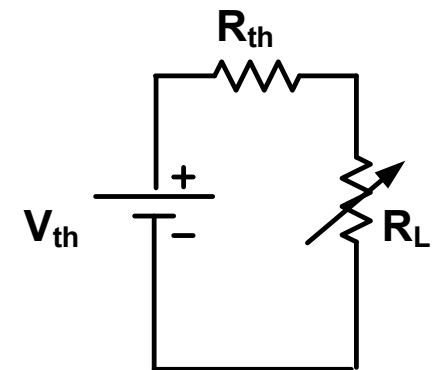


Maximum power transfer theorem (when R_L varies)

1. When $R_L = R_{th}$

$$2. P_{Lmax} = \frac{V_{th}^2}{4R_{th}}$$


Power transfer efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{R_L}{R_L + R_{th}}$$

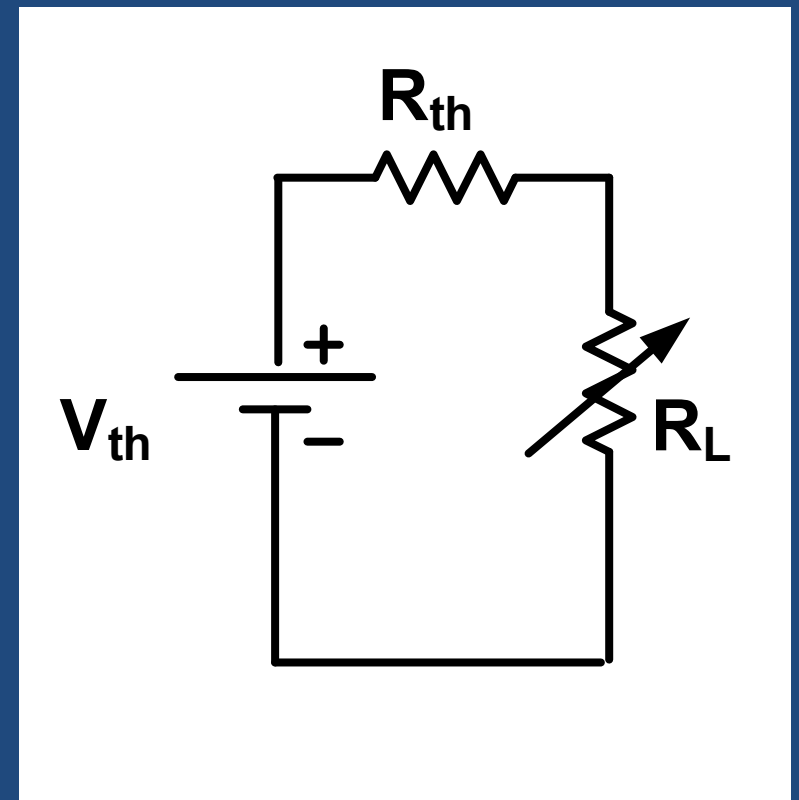


Example 20

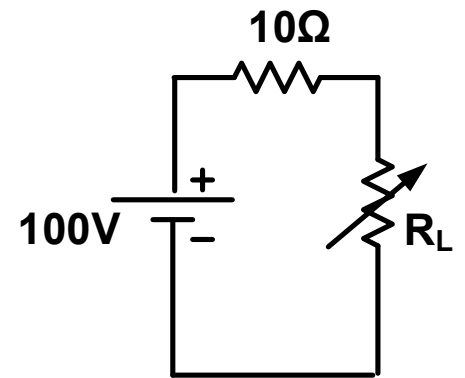1. Find $P_{L_{\max}}$
2. If $P_L = 160\text{W}$ find R_L and η



Solution of example 20

- $P_{Lmax} = \frac{100^2}{4 \cdot 10} = 250 \text{ W}$
- $P_L = R_L I^2$
- $= R_L \left(\frac{100}{10 + R_L} \right)^2 = 160$
- or $R_L^2 - 42.5 R_L + 100 = 0$
- \Rightarrow Solutions: $R_L = 40\Omega$ and 2.5Ω
- $\eta = \frac{R_L}{R_L + R_{th}}$
 - For $R_L = 40\Omega \Rightarrow \eta_1 = \frac{40}{40 + 10} 100 = 80\%$
 - For $R_L = 2.5\Omega \Rightarrow \eta_2 = \frac{2.5}{2.5 + 10} 100 = 20\%$
- \Rightarrow Take $R_L = 40\Omega$ to have $\eta = 80\%$ for the same power.

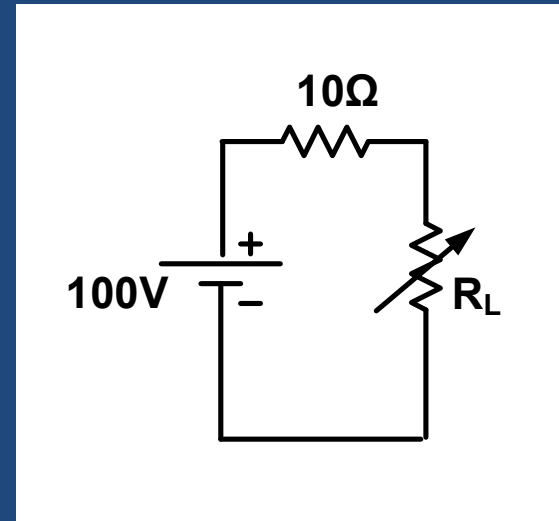



Võ Văn Tới
School of Biomedical Engineering
International University of Vietnam National Universities
HCM City, Vietnam
Email: vvtoi@hcmiu.edu.vn
Website: www.hcmiu.edu.vn/bme

